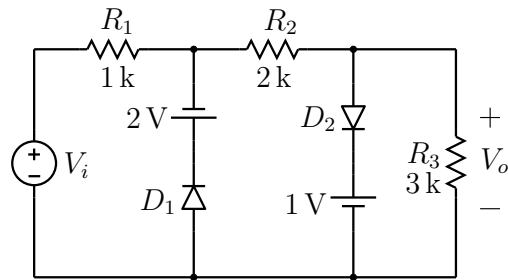


EE 112 Mid-Sem Exam (MBP)  
(Feb. 23, 2017)

1. In the circuit shown in the figure, assume that the diodes have  $V_{on} = 0.7\text{ V}$ .
- (a) Find the range of  $V_i$  for which (i) only  $D_1$  conducts, (ii) only  $D_2$  conducts, (iii) both  $D_1$  and  $D_2$  conduct, (iv) neither  $D_1$  nor  $D_2$  conducts.
  - (b) Calculate the slope  $\frac{dV_o}{dV_i}$  in each of the above regions.
  - (c) Plot  $V_o$  versus  $V_i$  for  $-10\text{ V} < V_i < 10\text{ V}$ , showing clearly the voltage levels, break points, and slopes. [6]




2. Consider a logical function  $X$  of four variables  $A_3, A_1, A_2, A_0$ . Let  $d$  be the decimal number corresponding to the binary number  $A_3A_1A_2A_0$ .  $X$  is 1 if either of the following conditions is met. (i)  $d \leq 7$ , (ii) The number of 1's in the input variables is odd.
- (a) Write the truth table for  $X$ .
  - (b) Write  $X$  in the standard product-of-sums form. [4]
3. Implement the function  $Y = A \bar{B} C + \bar{C} D$  using
- (a) an 8-to-1 MUX,
  - (b) only 2-input NAND gates,
  - (c) only 2-input NOR gates. [6]

4. We want to design a synchronous counter with the state transition table given in the figure.

- Write the transition table for a  $JK$  flip-flop (i.e., a table showing  $J$ ,  $K$ ,  $Q_{n+1}$ ).
- From the above table, construct a table showing  $Q_n$ ,  $Q_{n+1}$ ,  $J$ ,  $K$ , where the  $J$  and  $K$  values for all possible transitions (from  $Q_n$  to  $Q_{n+1}$ ) are listed. Explain how you obtained *one* of the entries.
- Using the above table and the counter state transition table, prepare K-maps for  $J_1$  and  $K_1$  (K-maps for  $J_0$ ,  $K_0$ ,  $J_2$ ,  $K_2$ ,  $J_3$ ,  $K_3$  are not required).
- From the K-maps, obtain minimal expressions for  $J_1$  and  $K_1$ .

(No marks for writing the answers by any other method.)

[8]

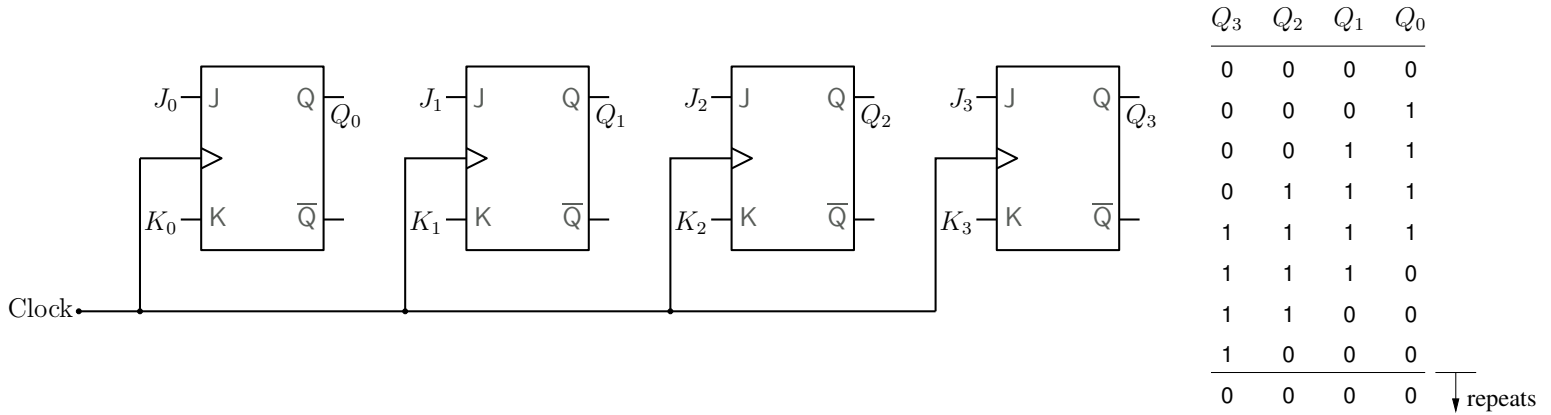

5. The capacitor in the figure is initially uncharged, and a pulse  $V_s(t)$  shown in the figure is applied. Assume that the diodes have  $V_{on} = 0.7 \text{ V}$ .

- Sketch  $V_o(t)$  to scale, showing all salient features, including time points and voltage levels. Justify your answer with calculations.
- What is  $V_o$  at  $t = 2 \text{ msec}$ ?
- What is  $V_o$  at  $t = 15 \text{ msec}$ ?

[6]

