
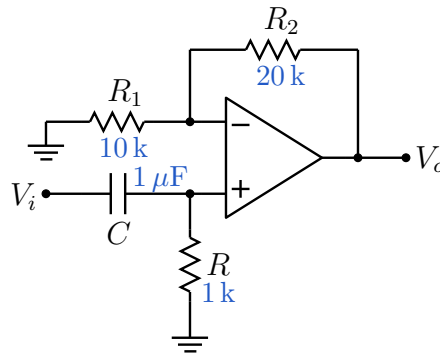


# EE 112 (MBP): HW 9 (April 10, 2017)

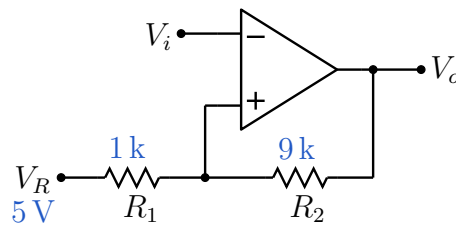1. For the op-amp filter shown in the figure, obtain an expression for the transfer function  $H(j\omega)$ . What type of filter is this? What is its corner frequency?



2. For the Schmitt shown in the figure, find the threshold points  $V_{TH}$  and  $V_{TL}$ . Plot  $V_o$  versus  $V_i$ . ( $\pm V_{sat} = \pm 12\text{ V}$ )



3. The circuit shown in the figure is used to solve an ODE (ordinary differential equation) of the form  $\frac{dV}{dt} = f(V_i, V)$ . Find the ODE. Assume that all Op Amps are operating in the linear regime.

