
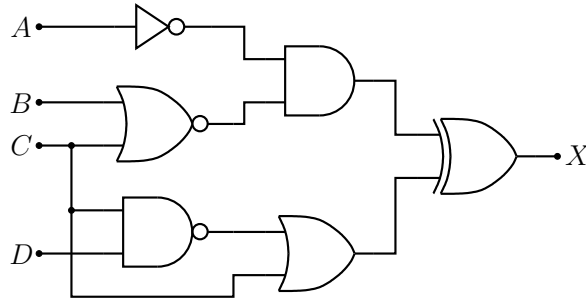


EE 112 (MBP): HW 1 (January 2017)

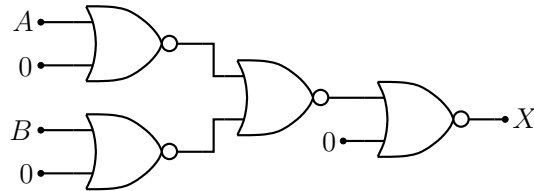
- Construct truth tables for $X_1 = \overline{A}B + A\overline{B}$ and $X_2 = \overline{A}\overline{B}(A + B)$, and show that they are equivalent.
- Write the Boolean expression for X . Simplify the expression and determine the conditions for which $X = 0$.



- Write the Boolean expression for X , and construct its truth table.



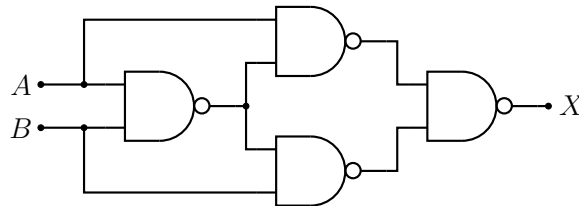- (a) Show that $\overline{A} + AB = \overline{A} + B$. (b) Using this identity, simplify the expression for the output X in the figure. What function is this circuit performing?



- Implement the function $Y = \overline{A}(B + C) + D$ using (a) only NAND gates, (b) only NOR gates.
- Implement the function in Q 5 using (i) a 16-to-1 MUX, (ii) an 8-to-1 MUX.
- Minimise the functions Y_1 , Y_2 , Y_3 given by the following K-maps.

CD \ AB	AB			
	00	01	11	10
00	1	1	1	1
01	1	X	0	0
11	0	0	X	1
10	0	1	1	0

Y_1

CD \ AB	AB			
	00	01	11	10
00	X	0	1	1
01	1	0	0	1
11	0	0	0	0
10	1	0	1	1

Y_2

C \ AB	AB			
	00	01	11	10
0	X	0	1	1
1	1	0	0	1

Y_3