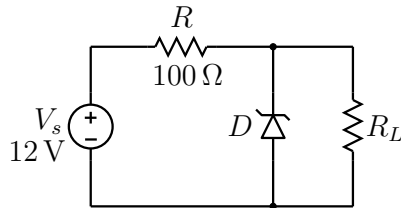



# EE 112 (MBP): HW 4 (February 13, 2017)

- Shown in the figure is a simple voltage regulator which is meant to maintain a constant voltage at the output, irrespective of the load resistance value (as long as it falls in a certain range). The Zener diode has  $V_Z = 5.6 \text{ V}$ .

- For  $R_L = 150 \Omega$ , what is the current through the Zener diode?
- What is the minimum value of  $R_L$  for which the circuit will work as desired?



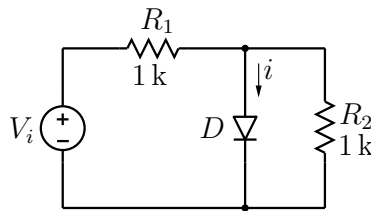
- For the circuit shown in the figure, plot  $i$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ . ( $V_{\text{on}} = 0.7 \text{ V}$  for the diode.)



- Assume that the diodes in the following circuit are ideal (with  $V_{\text{on}} = 0 \text{ V}$ ).

- What is the condition on  $V_i$  for  $D_2$  to be on and  $D_1$  to be off?
- What is the condition on  $V_i$  for  $D_1$  to be on and  $D_2$  to be off?
- Plot  $i$  versus  $V_i$  for  $0 \text{ V} < V_i < 25 \text{ V}$ .
- Repeat for  $V_{\text{on}} = 0.7 \text{ V}$ .

(Source: Millman)

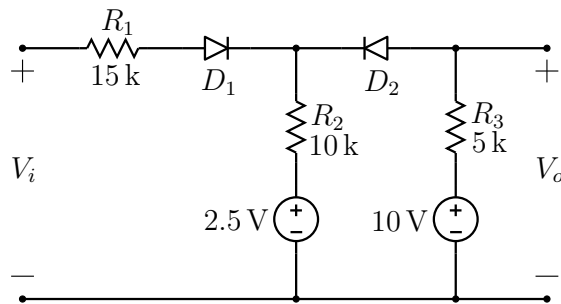

4. The  $V_o$  versus  $V_i$  relationship for a circuit is given in the figure. The circuit has one diode with  $V_{on} = 0.7\text{ V}$ , and two resistors  $R_1$  and  $R_2$ . One of the resistances is  $1\text{ k}\Omega$ . Draw the circuit and find the other resistance.

