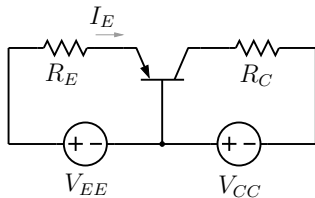


## EE 112-2016 Tutorial 2 (MBP/JJ)

**Note:** For *nnp* transistors, assume  $V_{BE} = 0.7\text{ V}$  in active and saturation regions, and  $V_{CE}^{\text{sat}} = 0.2\text{ V}$ . For *pnp* transistors, the same numbers correspond to  $V_{EB}$  and  $V_{EC}^{\text{sat}}$ , respectively.


- In the circuit shown in the figure,  $V_{CC}$  and  $V_{EE}$  are 5 V each. Assume that the transistor is in the active region, and  $\alpha \approx 1$ .

- Find  $R_E$  such that  $I_E = 2\text{ mA}$ .
- Given that  $I_E = 2\text{ mA}$ , find  $R_C$  such that  $V_{BC} = 1\text{ V}$ .
- Given that  $I_E = 2\text{ mA}$ , find the maximum value of  $R_C$  such that the transistor is in the active region. (Reference: Bobrow)




- In the current source circuit shown in the figure,  $V_Z = 5.1\text{ V}$ .

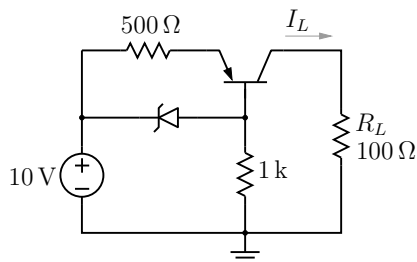
- Find  $I_L$  (neglect base current).
- What is the range of  $R_L$  for which the current delivered to the load is  $I_L$ ?



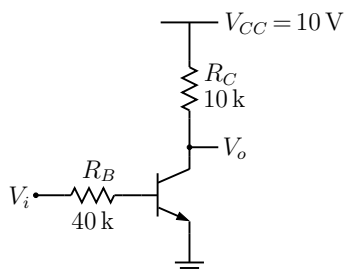
- A BJT inverter is shown in the figure. Sketch  $V_o$  versus  $V_i$  for  $0 < V_i < 10\text{ V}$  with (a)  $\beta = 40$ , (b)  $\beta = 80$ .



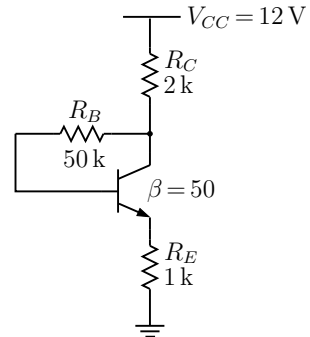
- For the BJT circuit shown in the figure, find  $I_C$  and  $V_{CE}$ . What is the special feature of this circuit?



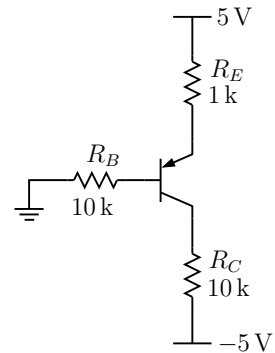- Find all voltages and currents if  $\beta = 30$ . (Reference: Sedra/Smith)




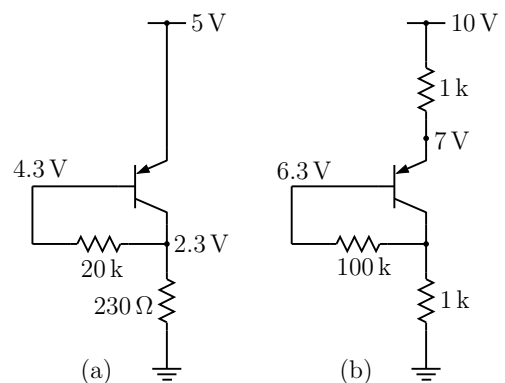- Measured voltages are shown. Find  $\beta$  in each case. (Reference: Sedra/Smith)



7. The transistor in the circuit shown in the figure has  $\beta = 100$ . The other parameters are  $R_1 = 60 \text{ k}\Omega$ ,  $R_2 = 30 \text{ k}\Omega$ ,  $R_C = 1 \text{ k}\Omega$ ,  $R_E = 100 \Omega$ ,  $V_{CC} = 6 \text{ V}$ .

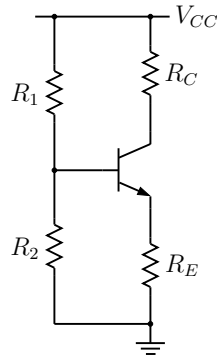- (a) Assuming that the transistor is operating in the active mode, find  $I_B$ ,  $I_C$ , and  $V_{CE}$ . Check if the assumption of active mode is correct.
- (b) What is the minimum value of  $R_E$  for the BJT to operate in the active mode?  
(Reference: Bobrow)



8. The transistor of P-7 has  $\beta = 100$ . Given  $R_1 = 60 \text{ k}\Omega$ ,  $R_2 = 30 \text{ k}\Omega$ ,  $V_{CC} = 6 \text{ V}$ , find  $R_C$  and  $R_E$  such that the BJT is biased in the active region with  $I_C = 2 \text{ mA}$ ,  $V_{CE} = 2.1 \text{ V}$ .  
(Reference: Bobrow)

9. A common-emitter amplifier is shown in the figure.

- (a) Draw the midband equivalent circuit.
- (b) Find  $v_o/v_i$ ,  $v_o/v_s$ ,  $R_{in}$ ,  $R_{out}$ , assuming  $\beta = 50$ ,  $V_T = 26 \text{ mV}$ .
- (c) Repeat if the bypass capacitor  $C_E$  is removed.

