

# Diode Circuits: Part 1

---





M. B. Patil

[mbpatil@ee.iitb.ac.in](mailto:mbpatil@ee.iitb.ac.in)

[www.ee.iitb.ac.in/~sequel](http://www.ee.iitb.ac.in/~sequel)

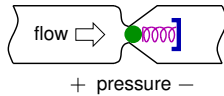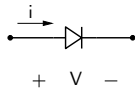Department of Electrical Engineering  
Indian Institute of Technology Bombay





- \* A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).



- \* A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).
- \* A check valve presents a small resistance if the pressure  $p > 0$ , but blocks the flow (i.e., presents a large resistance) if  $p < 0$ .





- \* A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).
- \* A check valve presents a small resistance if the pressure  $p > 0$ , but blocks the flow (i.e., presents a large resistance) if  $p < 0$ .
- \* Similarly, a diode presents a small resistance in the forward direction and a large resistance in the reverse direction.



- \* A diode may be thought of as the electrical counterpart of a directional valve (“check valve”).
- \* A check valve presents a small resistance if the pressure  $p > 0$ , but blocks the flow (i.e., presents a large resistance) if  $p < 0$ .
- \* Similarly, a diode presents a small resistance in the forward direction and a large resistance in the reverse direction.
- \* Note: In a practical diode, the resistance  $R_D = V/i$  is a nonlinear function of the applied voltage  $V$ . However, it is often a good approximation to treat it as a constant resistance which is small if  $V$  is positive and large if  $V$  is negative.

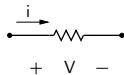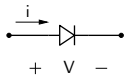
## Simple models: $R_{\text{on}}/R_{\text{off}}$ model



$$R = R_{\text{on}} \text{ if } V > 0$$

$$R = R_{\text{off}} \text{ if } V < 0$$

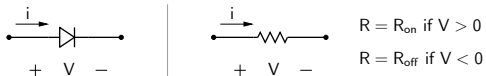
## Simple models: $R_{\text{on}}/R_{\text{off}}$ model



- \* Since the resistance is different in the forward and reverse directions, the  $i - V$  relationship is not a straight line.




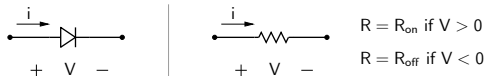
## Simple models: $R_{\text{on}}/R_{\text{off}}$ model



- \* Since the resistance is different in the forward and reverse directions, the  $i - V$  relationship is not a straight line.
- \* Examples:

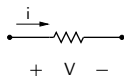
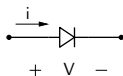
## Simple models: $R_{\text{on}}/R_{\text{off}}$ model




$$R = R_{\text{on}} \text{ if } V > 0$$


$$R = R_{\text{off}} \text{ if } V < 0$$

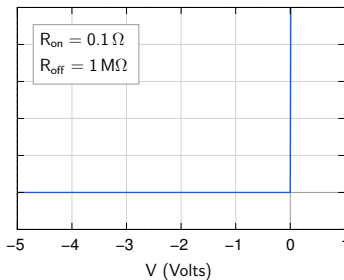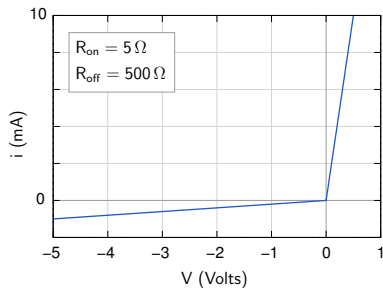- \* Since the resistance is different in the forward and reverse directions, the  $i - V$  relationship is not a straight line.
- \* Examples:




## Simple models: ideal switch

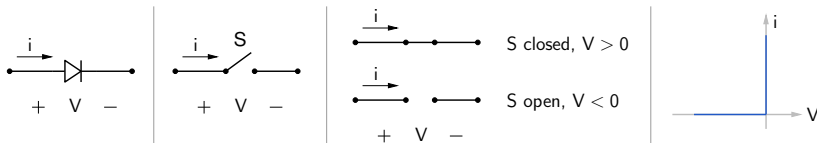


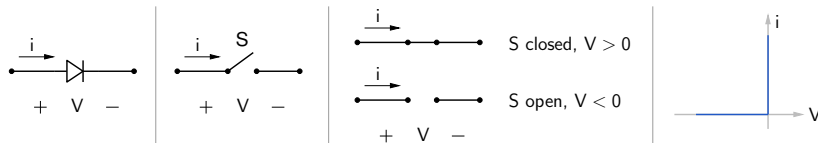

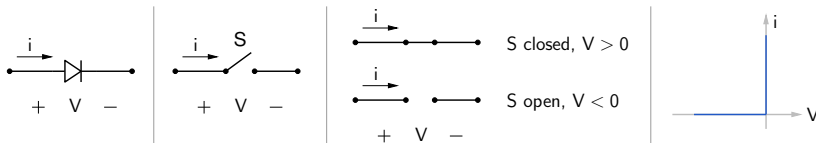\* Forward bias:  $i > 0$  A,  $V = 0$  V,  $\rightarrow$  S is closed (a perfect contact).




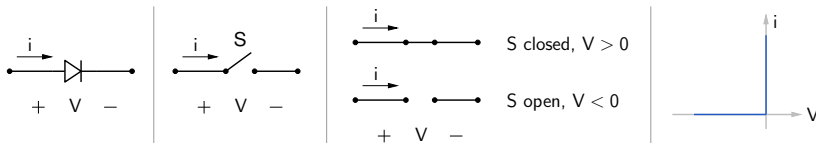
- \* Forward bias:  $i > 0\text{ A}$ ,  $V = 0\text{ V}$ ,  $\rightarrow S$  is closed (a perfect contact).
- \* Reverse bias:  $V < 0\text{ V}$ ,  $i = 0\text{ A} \rightarrow S$  is open (a perfect open circuit). The diode is said to “block” the reverse applied voltage.



- \* Forward bias:  $i > 0$  A,  $V = 0$  V,  $\rightarrow$   $S$  is closed (a perfect contact).
- \* Reverse bias:  $V < 0$  V,  $i = 0$  A  $\rightarrow$   $S$  is open (a perfect open circuit). The diode is said to “block” the reverse applied voltage.
- \* The actual values of  $V$  and  $i$  for a diode in a circuit get determined by the  $i$ - $V$  relationship of the diode *and* the constraints on  $V$  and  $i$  imposed by the circuit.

# Shockley diode equation

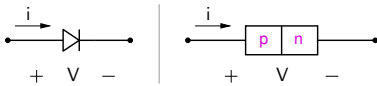

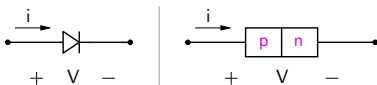

$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$


$k_B$  = Boltzmann's constant =  $1.38 \times 10^{-23} \text{ J/K}$ .

$q$  = electron charge =  $1.602 \times 10^{-19} \text{ Coul}$ .

$T$  = temperature in  $^{\circ}\text{K}$ .

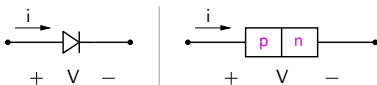$V_T \approx 25 \text{ mV}$  at room temperature ( $27^{\circ}\text{C}$ ).





$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$


$k_B$  = Boltzmann's constant =  $1.38 \times 10^{-23} \text{ J/K}$ .

$q$  = electron charge =  $1.602 \times 10^{-19} \text{ Coul}$ .

$T$  = temperature in  $^{\circ}\text{K}$ .

$V_T \approx 25 \text{ mV}$  at room temperature ( $27^{\circ}\text{C}$ ).

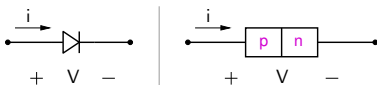\*  $I_s$  is called the "reverse saturation current."



$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$


$k_B$  = Boltzmann's constant =  $1.38 \times 10^{-23} \text{ J/K}$ .

$q$  = electron charge =  $1.602 \times 10^{-19} \text{ Coul}$ .

$T$  = temperature in  $^{\circ}\text{K}$ .

$V_T \approx 25 \text{ mV}$  at room temperature ( $27^{\circ}\text{C}$ ).

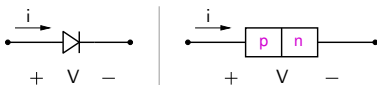- \*  $I_s$  is called the “reverse saturation current.”
- \* For a typical low-power silicon diode,  $I_s$  is of the order of  $10^{-13} \text{ A}$  (i.e., 0.1 pA).



$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$


$k_B$  = Boltzmann's constant =  $1.38 \times 10^{-23} \text{ J/K}$ .

$q$  = electron charge =  $1.602 \times 10^{-19} \text{ Coul}$ .

$T$  = temperature in  $^{\circ}\text{K}$ .

$V_T \approx 25 \text{ mV}$  at room temperature ( $27^{\circ}\text{C}$ ).

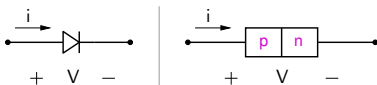- \*  $I_s$  is called the “reverse saturation current.”
- \* For a typical low-power silicon diode,  $I_s$  is of the order of  $10^{-13} \text{ A}$  (i.e., 0.1 pA).
- \* Although  $I_s$  is very small, it gets multiplied by a large exponential factor, giving a diode current of several mA for  $V \approx 0.7 \text{ V}$  in a silicon diode.



$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

$k_B$  = Boltzmann's constant =  $1.38 \times 10^{-23} \text{ J/K}$ .


$q$  = electron charge =  $1.602 \times 10^{-19} \text{ Coul}$ .

$T$  = temperature in  $^{\circ}\text{K}$ .

$V_T \approx 25 \text{ mV}$  at room temperature ( $27^{\circ}\text{C}$ ).

- \*  $I_s$  is called the “reverse saturation current.”
- \* For a typical low-power silicon diode,  $I_s$  is of the order of  $10^{-13} \text{ A}$  (i.e., 0.1 pA).
- \* Although  $I_s$  is very small, it gets multiplied by a large exponential factor, giving a diode current of several mA for  $V \approx 0.7 \text{ V}$  in a silicon diode.
- \* The “turn-on” voltage ( $V_{\text{on}}$ ) of a diode depends on the value of  $I_s$ .  $V_{\text{on}}$  may be defined as the voltage at which the diode starts carrying a substantial forward current (say, a few mA).  
For a silicon diode,  $V_{\text{on}} \approx 0.7 \text{ V}$ .  
For LEDs,  $V_{\text{on}}$  varies from about 1.8 V (red) to 3.3 V (blue).


## Shockley diode equation

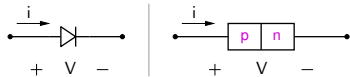

$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

Example:  $I_s = 1 \times 10^{-13} \text{ A}$ ,  $V_T = 25 \text{ mV}$ .

## Shockley diode equation

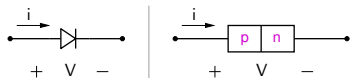


$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

Example:  $I_s = 1 \times 10^{-13} \text{ A}$ ,  $V_T = 25 \text{ mV}$ .

$V$	$x = V/V_T$	$e^x$	$i \text{ (Amp)}$
0.1	3.87	$0.479 \times 10^2$	$0.469 \times 10^{-11}$
0.2	7.74	$0.229 \times 10^4$	$0.229 \times 10^{-9}$
0.3	11.6	$0.110 \times 10^6$	$0.110 \times 10^{-7}$
0.4	15.5	$0.525 \times 10^7$	$0.525 \times 10^{-6}$
0.5	19.3	$0.251 \times 10^9$	$0.251 \times 10^{-4}$
0.6	23.2	$0.120 \times 10^{11}$	$0.120 \times 10^{-2}$
0.62	24.0	$0.260 \times 10^{11}$	$0.260 \times 10^{-2}$
0.64	24.8	$0.565 \times 10^{11}$	$0.565 \times 10^{-2}$
0.66	25.5	$0.122 \times 10^{12}$	$0.122 \times 10^{-1}$
0.68	26.3	$0.265 \times 10^{12}$	$0.265 \times 10^{-1}$
0.70	27.1	$0.575 \times 10^{12}$	$0.575 \times 10^{-1}$
0.72	27.8	$0.125 \times 10^{13}$	0.125


# Shockley diode equation

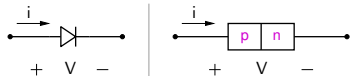



$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right], \text{ where } V_T = k_B T / q.$$

Example:  $I_s = 1 \times 10^{-13} \text{ A}$ ,  $V_T = 25 \text{ mV}$ .

$V$	$x = V/V_T$	$e^x$	$i \text{ (Amp)}$
0.1	3.87	$0.479 \times 10^2$	$0.469 \times 10^{-11}$
0.2	7.74	$0.229 \times 10^4$	$0.229 \times 10^{-9}$
0.3	11.6	$0.110 \times 10^6$	$0.110 \times 10^{-7}$
0.4	15.5	$0.525 \times 10^7$	$0.525 \times 10^{-6}$
0.5	19.3	$0.251 \times 10^9$	$0.251 \times 10^{-4}$
0.6	23.2	$0.120 \times 10^{11}$	$0.120 \times 10^{-2}$
0.62	24.0	$0.260 \times 10^{11}$	$0.260 \times 10^{-2}$
0.64	24.8	$0.565 \times 10^{11}$	$0.565 \times 10^{-2}$
0.66	25.5	$0.122 \times 10^{12}$	$0.122 \times 10^{-1}$
0.68	26.3	$0.265 \times 10^{12}$	$0.265 \times 10^{-1}$
0.70	27.1	$0.575 \times 10^{12}$	$0.575 \times 10^{-1}$
0.72	27.8	$0.125 \times 10^{13}$	0.125

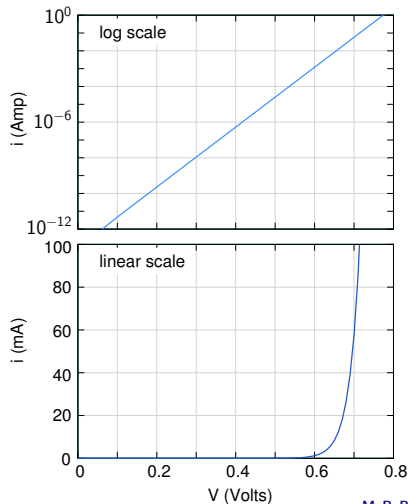



## Diode circuit model

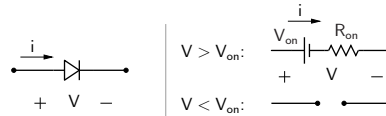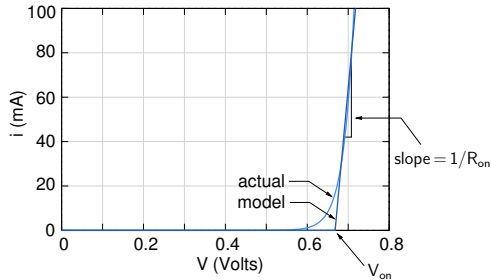

- \* In many circuits,  $R_{on}$  can be neglected (assumed to be  $0\Omega$ ) since it is much smaller than the other resistances in the circuit. In that case, the diode in forward conduction can be replaced with simply a battery.



# Diode circuit model

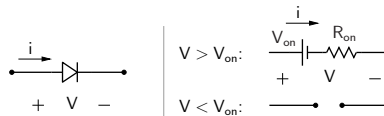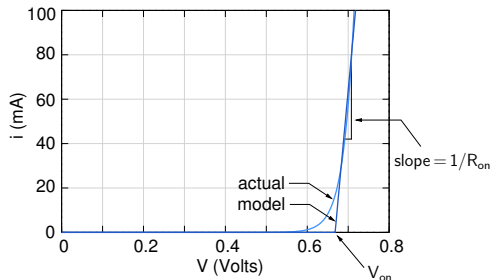


- \* In many circuits,  $R_{on}$  can be neglected (assumed to be  $0\ \Omega$ ) since it is much smaller than the other resistances in the circuit. In that case, the diode in forward conduction can be replaced with simply a battery.
- \* Note that the “battery” shown in the above model is not a “source” of power! It can only absorb power (see the direction of the current), causing heat dissipation.

- \* In DC situations, for each diode in the circuit, we need to establish whether it is on or off, replace it with the corresponding equivalent circuit, and then obtain the quantities of interest.


- \* In DC situations, for each diode in the circuit, we need to establish whether it is on or off, replace it with the corresponding equivalent circuit, and then obtain the quantities of interest.
- \* In transient analysis, we need to find the time points at which a diode turns on or off, and analyse the circuit in intervals between these time points.

- \* In DC situations, for each diode in the circuit, we need to establish whether it is on or off, replace it with the corresponding equivalent circuit, and then obtain the quantities of interest.
- \* In transient analysis, we need to find the time points at which a diode turns on or off, and analyse the circuit in intervals between these time points.
- \* In some diode circuits, the exponential nature of the diode I-V relationship (the Shockley model) is made use of. For these circuits, computation is usually difficult, and computer simulation may be required to solve the resulting non-linear equations.


## Diode circuit example

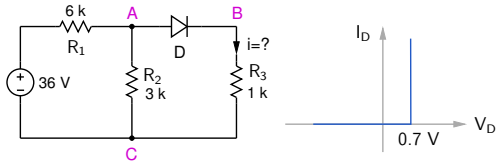


## Diode circuit example

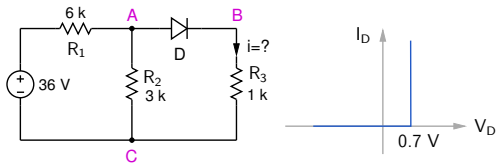


Case 1: D is off.

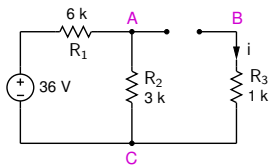

## Diode circuit example

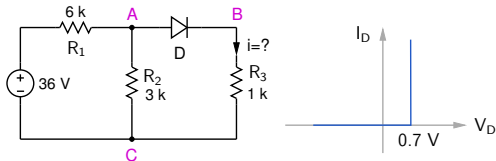


Case 1: D is off.

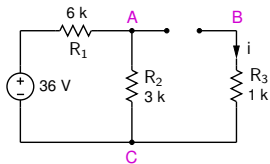


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$

which is not consistent with our assumption of D being off.

## Diode circuit example

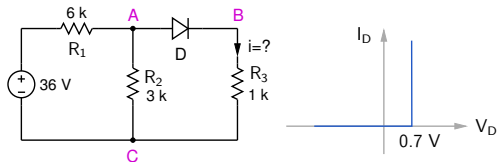

Case 1: D is off.

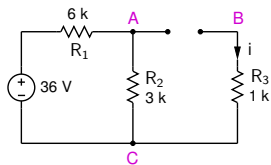



$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$

which is not consistent with our assumption of D being off.


→ D must be on.



## Diode circuit example

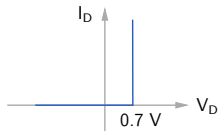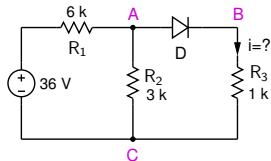

Case 1: D is off.

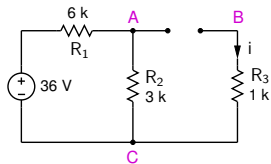


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$



which is not consistent with our assumption of D being off.

→ D must be on.


Case 2: D is on.

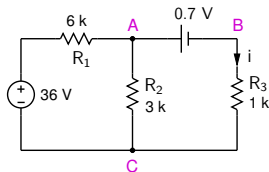

## Diode circuit example

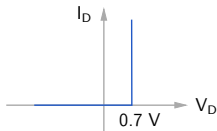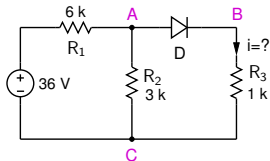

Case 1: D is off.

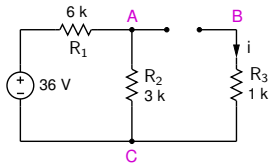


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$

which is not consistent with our assumption of D being off.

→ D must be on.

Case 2: D is on.


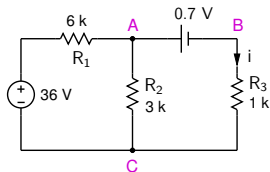


Taking  $V_C = 0 \text{ V}$ ,


$$\frac{V_A - 36}{6 \text{ k}} + \frac{V_A}{3 \text{ k}} + \frac{V_A - 0.7}{1 \text{ k}} = 0,$$

$$\rightarrow V_A = 4.47 \text{ V}, i = 3.77 \text{ mA}.$$

## Diode circuit example

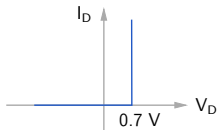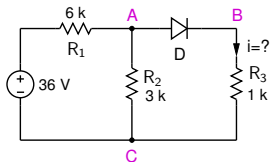

Case 1: D is off.

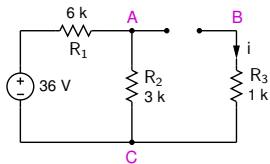


$$V_{AB} = V_{AC} = \frac{3}{9} \times 36 = 12 \text{ V},$$

which is not consistent with our assumption of D being off.

→ D must be on.

Case 2: D is on.

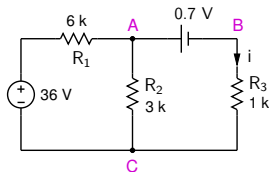



Taking  $V_C = 0 \text{ V}$ ,

$$\frac{V_A - 36}{6 \text{ k}} + \frac{V_A}{3 \text{ k}} + \frac{V_A - 0.7}{1 \text{ k}} = 0,$$

$$\rightarrow V_A = 4.47 \text{ V}, i = 3.77 \text{ mA}.$$



Remark: Often, we can figure out by inspection if a diode is on or off.

## Diode circuit example

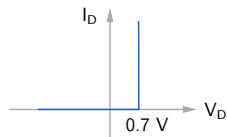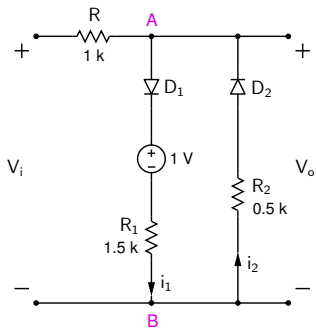

- (a) Plot  $V_o$  versus  $V_i$  for  $-5\text{ V} < V_i < 5\text{ V}$ .
- (b) Plot  $V_o(t)$  for a triangular input:  
 $-5\text{ V}$  to  $+5\text{ V}$ ,  $500\text{ Hz}$ .



## Diode circuit example

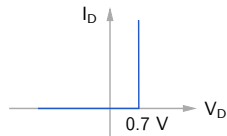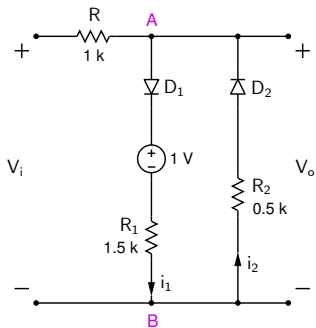

- (a) Plot  $V_o$  versus  $V_i$  for  $-5\text{ V} < V_i < 5\text{ V}$ .
- (b) Plot  $V_o(t)$  for a triangular input:  
 $-5\text{ V}$  to  $+5\text{ V}$ ,  $500\text{ Hz}$ .

First, let us show that  $D_1$  on  $\Rightarrow D_2$  off, and  $D_2$  on  $\Rightarrow D_1$  off.

## Diode circuit example

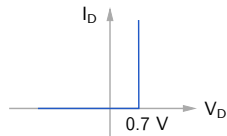
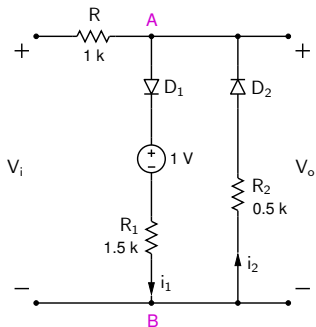


- (a) Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .
- (b) Plot  $V_o(t)$  for a triangular input:  
 $-5 \text{ V}$  to  $+5 \text{ V}$ ,  $500 \text{ Hz}$ .

First, let us show that  $D_1 \text{ on} \Rightarrow D_2 \text{ off}$ , and  $D_2 \text{ on} \Rightarrow D_1 \text{ off}$ .

Consider  $D_1$  to be on  $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$ .

## Diode circuit example

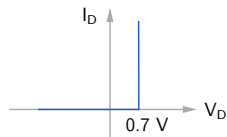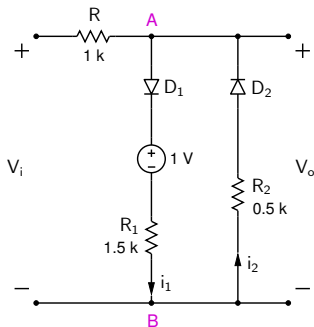

(a) Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .

(b) Plot  $V_o(t)$  for a triangular input:  
 $-5 \text{ V}$  to  $+5 \text{ V}$ ,  $500 \text{ Hz}$ .



First, let us show that  $D_1 \text{ on} \Rightarrow D_2 \text{ off}$ , and  $D_2 \text{ on} \Rightarrow D_1 \text{ off}$ .

Consider  $D_1$  to be on  $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$ .

Note that  $i_1 > 0$ , since  $D_1$  can only conduct in the forward direction.

$\Rightarrow V_{AB} > 1.7 \text{ V} \Rightarrow D_2$  cannot conduct.

## Diode circuit example

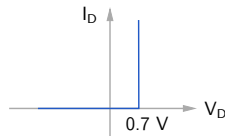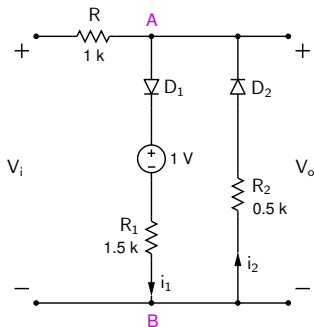

(a) Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .

(b) Plot  $V_o(t)$  for a triangular input:  
 $-5 \text{ V}$  to  $+5 \text{ V}$ ,  $500 \text{ Hz}$ .

First, let us show that  $D_1 \text{ on} \Rightarrow D_2 \text{ off}$ , and  $D_2 \text{ on} \Rightarrow D_1 \text{ off}$ .

Consider  $D_1$  to be on  $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$ .



Note that  $i_1 > 0$ , since  $D_1$  can only conduct in the forward direction.

$\Rightarrow V_{AB} > 1.7 \text{ V} \Rightarrow D_2$  cannot conduct.

Similarly, if  $D_2$  is on,  $V_{BA} > 0.7 \text{ V}$ , i.e.,  $V_{AB} < -0.7 \text{ V} \Rightarrow D_1$  cannot conduct.



## Diode circuit example

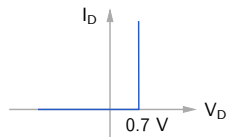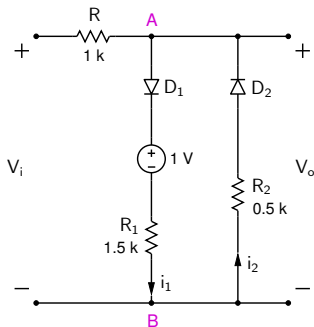

(a) Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .

(b) Plot  $V_o(t)$  for a triangular input:  
 $-5 \text{ V}$  to  $+5 \text{ V}$ ,  $500 \text{ Hz}$ .

First, let us show that  $D_1$  on  $\Rightarrow D_2$  off, and  $D_2$  on  $\Rightarrow D_1$  off.

Consider  $D_1$  to be on  $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$ .


Note that  $i_1 > 0$ , since  $D_1$  can only conduct in the forward direction.

$\Rightarrow V_{AB} > 1.7 \text{ V} \Rightarrow D_2$  cannot conduct.


Similarly, if  $D_2$  is on,  $V_{BA} > 0.7 \text{ V}$ , i.e.,  $V_{AB} < -0.7 \text{ V} \Rightarrow D_1$  cannot conduct.

Clearly,  $D_1$  on  $\Rightarrow D_2$  off, and  $D_2$  on  $\Rightarrow D_1$  off.

## Diode circuit example

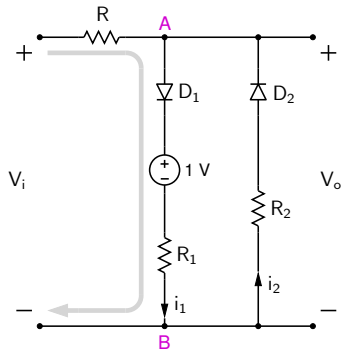


## Diode circuit example

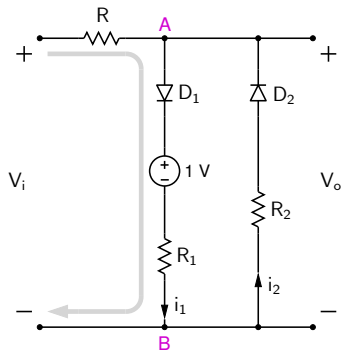

D<sub>1</sub> on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

## Diode circuit example

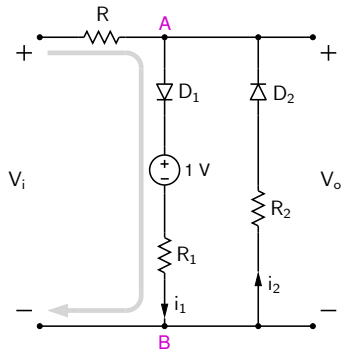


$D_1$  on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since  $i_1 > 0$ ,  $V_i > 1.7\text{ V}$


## Diode circuit example

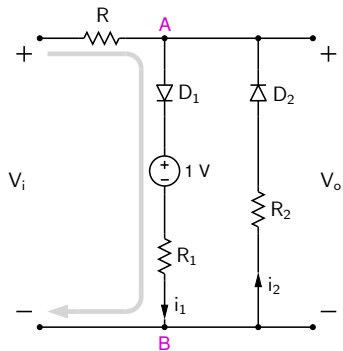


$D_1$  on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

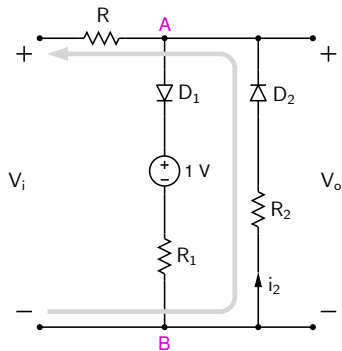Since  $i_1 > 0$ ,  $V_i > 1.7 \text{ V}$




## Diode circuit example

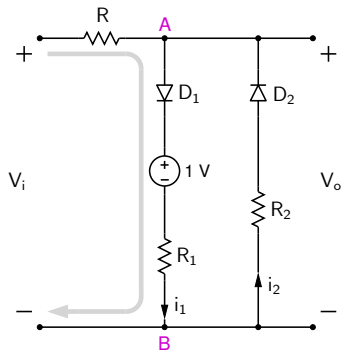

$D_1$  on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$


Since  $i_1 > 0$ ,  $V_i > 1.7\text{V}$

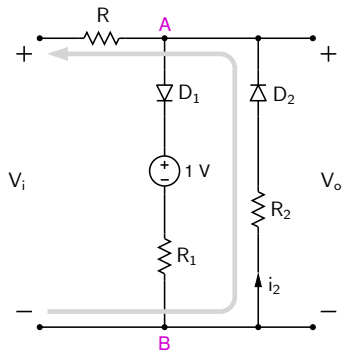

$D_2$  on:

$$i_2(R + R_2) + 0.7 + V_i = 0$$


## Diode circuit example

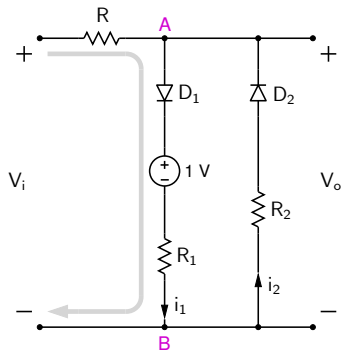

$D_1$  on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since  $i_1 > 0$ ,  $V_i > 1.7\text{V}$

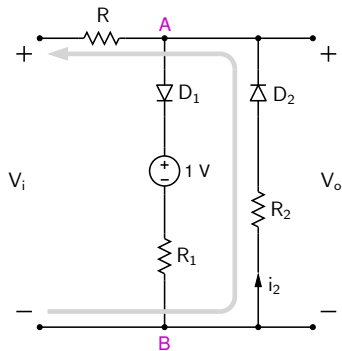


$D_2$  on:

$$i_2(R + R_2) + 0.7 + V_i = 0$$

$$V_i = -[0.7 + i_2(R + R_2)]$$


## Diode circuit example

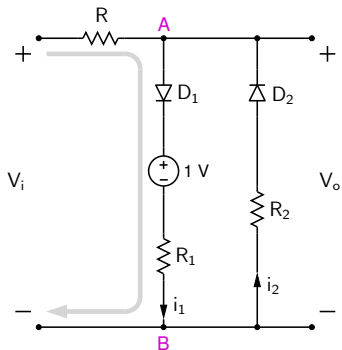

$D_1$  on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$

Since  $i_1 > 0$ ,  $V_i > 1.7\text{ V}$

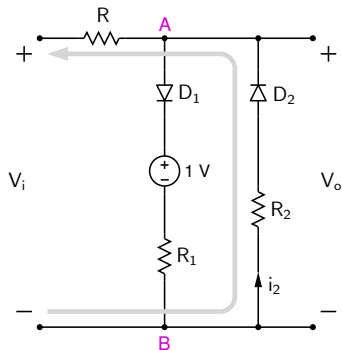

$D_2$  on:


$$i_2(R + R_2) + 0.7 + V_i = 0$$

$$V_i = -[0.7 + i_2(R + R_2)]$$

Since  $i_2 > 0$ ,  $V_i < -0.7\text{ V}$




## Diode circuit example

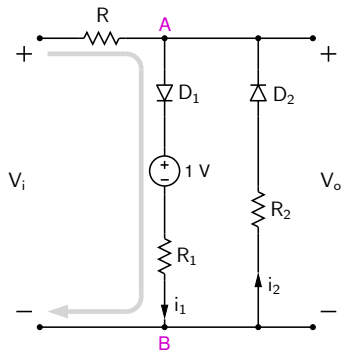

$D_1$  on:

$$V_i = i_1(R + R_1) + 1 + 0.7$$
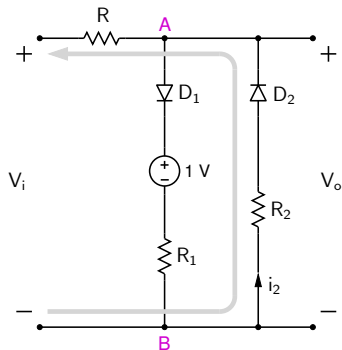
$$\text{Since } i_1 > 0, \boxed{V_i > 1.7\text{ V}}$$



$D_2$  on:


$$i_2(R + R_2) + 0.7 + V_i = 0$$

$$V_i = -[0.7 + i_2(R + R_2)]$$



$$\text{Since } i_2 > 0, \boxed{V_i < -0.7\text{ V}}$$

For  $-0.7\text{ V} < V_i < 1.7\text{ V}$ , neither  $D_1$  nor  $D_2$  can conduct.

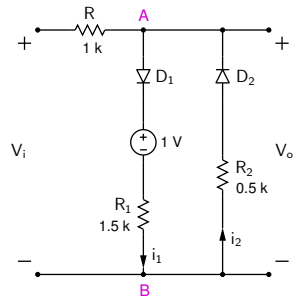- \* For  $-0.7\text{ V} < V_i < 1.7\text{ V}$ , both  $D_1$  and  $D_2$  are off.  
→ no drop across  $R$ , and  $V_o = V_i$ . (1)



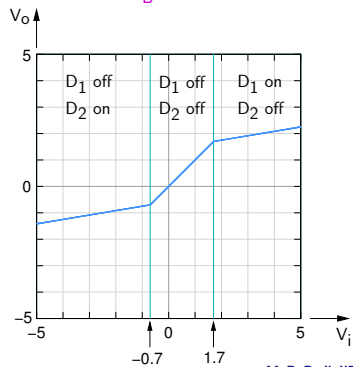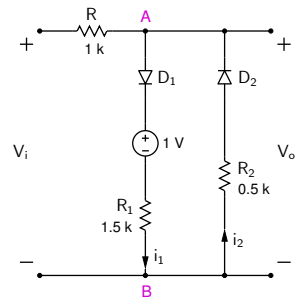- \* For  $-0.7\text{ V} < V_i < 1.7\text{ V}$ , both  $D_1$  and  $D_2$  are off.  
 $\rightarrow$  no drop across  $R$ , and  $V_o = V_i$ . (1)





\* For  $-0.7 \text{ V} < V_i < 1.7 \text{ V}$ , both  $D_1$  and  $D_2$  are off.  
 $\rightarrow$  no drop across  $R$ , and  $V_o = V_i$ . (1)

\* For  $V_i < -0.7 \text{ V}$ ,  $D_2$  conducts.  $\rightarrow V_o = -0.7 - i_2 R_2$ .  
 Use KVL to get  $i_2$ :  $V_i + i_2 R_2 + 0.7 + R i_2 = 0$ .

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$

$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}. \quad (2)$$
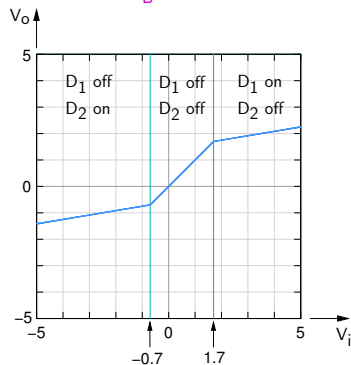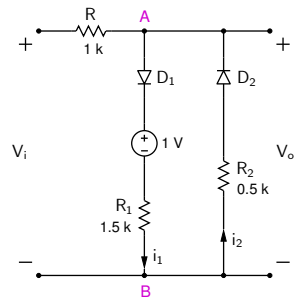
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_2}{R + R_2} = \frac{0.5 \text{ k}}{1 \text{ k} + 0.5 \text{ k}} = \frac{1}{3}.$$



- \* For  $-0.7 \text{ V} < V_i < 1.7 \text{ V}$ , both  $D_1$  and  $D_2$  are off.  
 $\rightarrow$  no drop across  $R$ , and  $V_o = V_i$ . (1)

- \* For  $V_i < -0.7 \text{ V}$ ,  $D_2$  conducts.  $\rightarrow V_o = -0.7 - i_2 R_2$ .  
 Use KVL to get  $i_2$ :  $V_i + i_2 R_2 + 0.7 + R i_2 = 0$ .

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$

$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}. \quad (2)$$



$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_2}{R + R_2} = \frac{0.5 \text{ k}}{1 \text{ k} + 0.5 \text{ k}} = \frac{1}{3}.$$

- \* For  $V_i > 1.7 \text{ V}$ ,  $D_1$  conducts.  $\rightarrow V_o = 0.7 + 1 + i_1 R_1$ .  
 Use KVL to get  $i_1$ :  $-V_i + i_1 R + 0.7 + 1 + i_1 R_1 = 0$ .

$$\rightarrow i_1 = \frac{V_i - 1.7}{R + R_1}, \text{ and}$$

$$V_o = 1.7 + R_1 i_1 = \frac{R_1}{R + R_1} V_i + 1.7 \frac{R}{R + R_1}. \quad (3)$$
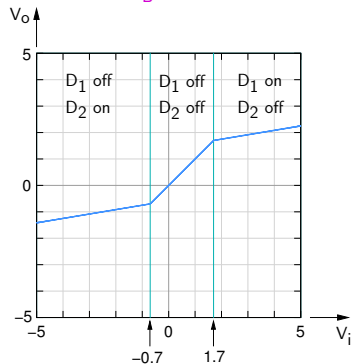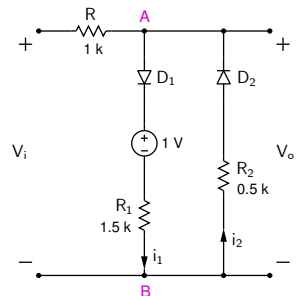
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1.5 \text{ k}}{1 \text{ k} + 1.5 \text{ k}} = \frac{3}{5}.$$



- \* For  $-0.7 \text{ V} < V_i < 1.7 \text{ V}$ , both  $D_1$  and  $D_2$  are off.  
 $\rightarrow$  no drop across  $R$ , and  $V_o = V_i$ . (1)

- \* For  $V_i < -0.7 \text{ V}$ ,  $D_2$  conducts.  $\rightarrow V_o = -0.7 - i_2 R_2$ .  
 Use KVL to get  $i_2$ :  $V_i + i_2 R_2 + 0.7 + R i_2 = 0$ .

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$

$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}. \quad (2)$$

$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_2}{R + R_2} = \frac{0.5 \text{ k}}{1 \text{ k} + 0.5 \text{ k}} = \frac{1}{3}.$$



- \* For  $V_i > 1.7 \text{ V}$ ,  $D_1$  conducts.  $\rightarrow V_o = 0.7 + 1 + i_1 R_1$ .  
 Use KVL to get  $i_1$ :  $-V_i + i_1 R + 0.7 + 1 + i_1 R_1 = 0$ .


$$\rightarrow i_1 = \frac{V_i - 1.7}{R + R_1}, \text{ and}$$

$$V_o = 1.7 + R_1 i_1 = \frac{R_1}{R + R_1} V_i + 1.7 \frac{R}{R + R_1}. \quad (3)$$

$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1.5 \text{ k}}{1 \text{ k} + 1.5 \text{ k}} = \frac{3}{5}.$$

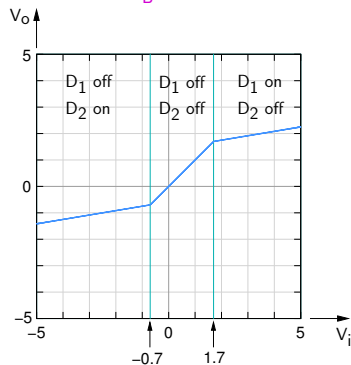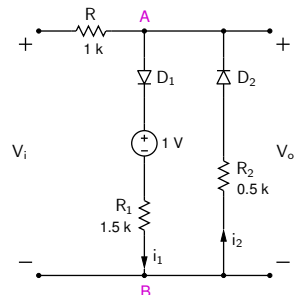
- \* Using Eqs. (1)-(3), we plot  $V_o$  versus  $V_i$ .  
 (SEQUEL file: ee101\_diode\_circuit\_1.sqproj)



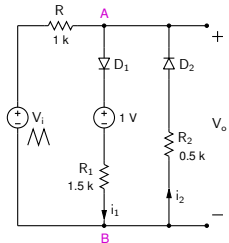


Point-by-point construction of  $V_o$  versus  $t$ :

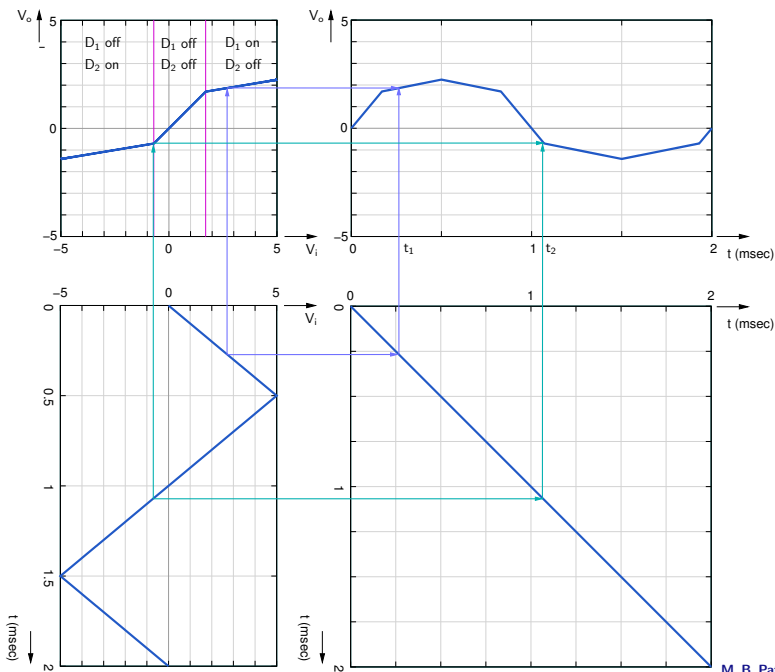Two time points,  $t_1$  and  $t_2$ , are shown as examples.




## Diode circuit example

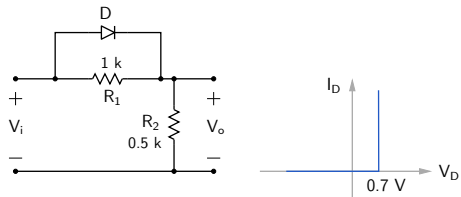


Plot  $V_o$  versus  $V_i$  for  $-5\text{ V} < V_i < 5\text{ V}$ .



## Diode circuit example

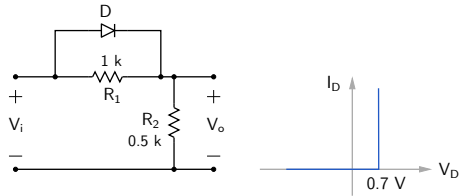


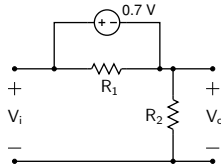Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .




D on  
 $V_o = V_i - 0.7$


## Diode circuit example

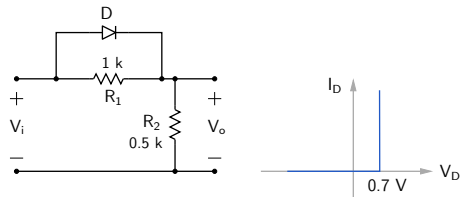

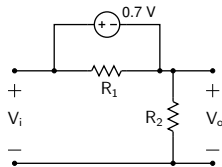Plot  $V_o$  versus  $V_i$  for  $-5\text{ V} < V_i < 5\text{ V}$ .




D on  
 $V_o = V_i - 0.7$

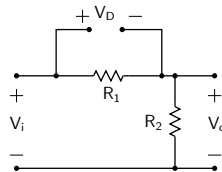


D off  
 $V_o = \frac{R_2}{R_1 + R_2} V_i$


## Diode circuit example

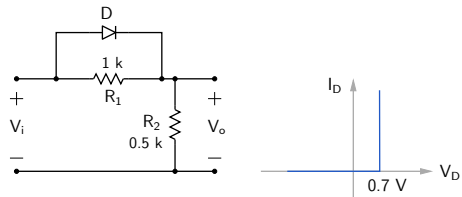

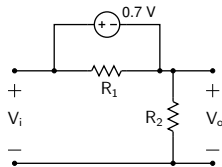Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .




D on  
 $V_o = V_i - 0.7$

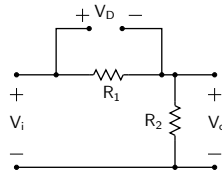


D off  
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of  $V_i$  will the diode turn on?


## Diode circuit example

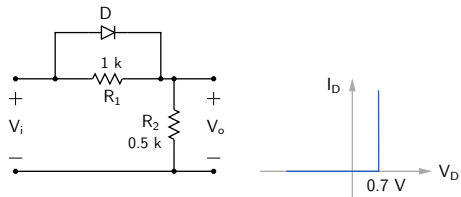

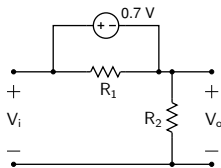Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .



D on  
 $V_o = V_i - 0.7$

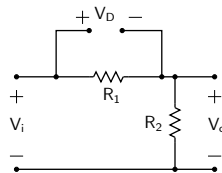


D off  
 $V_o = \frac{R_2}{R_1 + R_2} V_i$


At what value of  $V_i$  will the diode turn on?

In the off state,  $V_D = \frac{R_1}{R_1 + R_2} V_i$ .


## Diode circuit example

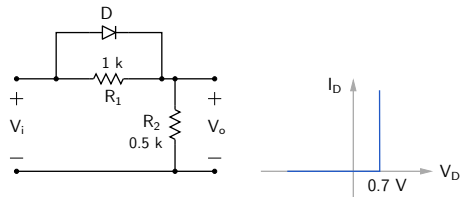

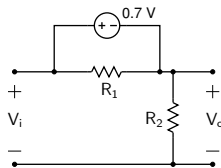Plot  $V_o$  versus  $V_i$  for  $-5\text{ V} < V_i < 5\text{ V}$ .



D on  
 $V_o = V_i - 0.7$

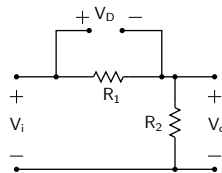

D off  
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of  $V_i$  will the diode turn on?


In the off state,  $V_D = \frac{R_1}{R_1 + R_2} V_i$ .

As  $V_i$  increases,  $V_D$  increases.


For  $D$  to turn on, we need  $V_D = 0.7\text{ V}$ .

i.e.,  $V_i = \frac{R_1 + R_2}{R_1} \times 0.7 = 1.05\text{ V}$ .


## Diode circuit example

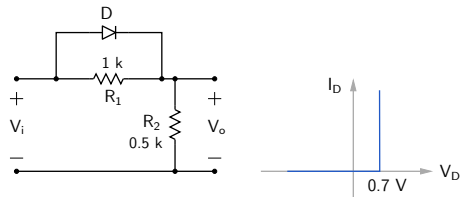

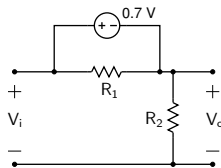Plot  $V_o$  versus  $V_i$  for  $-5\text{ V} < V_i < 5\text{ V}$ .



D on  
 $V_o = V_i - 0.7$

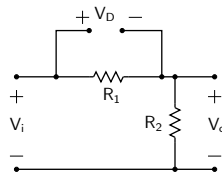

D off  
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of  $V_i$  will the diode turn on?

In the off state,  $V_D = \frac{R_1}{R_1 + R_2} V_i$ .


As  $V_i$  increases,  $V_D$  increases.

For  $D$  to turn on, we need  $V_D = 0.7\text{ V}$ .


i.e.,  $V_i = \frac{R_1 + R_2}{R_1} \times 0.7 = 1.05\text{ V}$ .

(SEQUEL file: ee101\_diode\_circuit\_2.sqproj)


## Diode circuit example

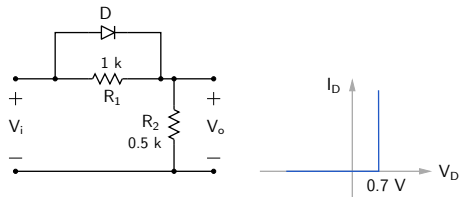

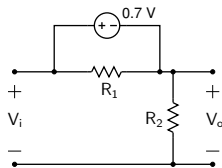Plot  $V_o$  versus  $V_i$  for  $-5\text{ V} < V_i < 5\text{ V}$ .



D on  
 $V_o = V_i - 0.7$

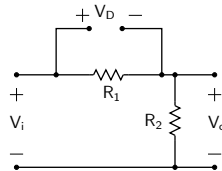

D off  
 $V_o = \frac{R_2}{R_1 + R_2} V_i$

At what value of  $V_i$  will the diode turn on?


In the off state,  $V_D = \frac{R_1}{R_1 + R_2} V_i$ .

As  $V_i$  increases,  $V_D$  increases.


For  $D$  to turn on, we need  $V_D = 0.7\text{ V}$ .

i.e.,  $V_i = \frac{R_1 + R_2}{R_1} \times 0.7 = 1.05\text{ V}$ .

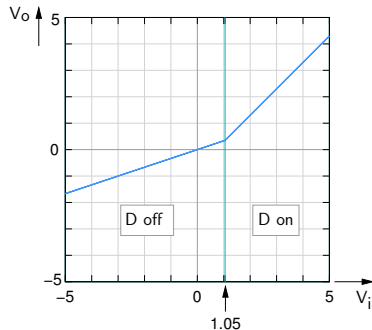
(SEQUEL file: ee101\_diode\_circuit\_2.sqproj)



## Diode circuit example

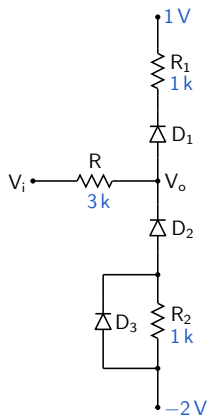


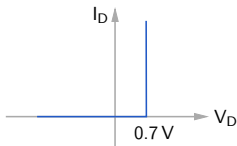Plot  $V_o$  versus  $V_i$  (Ref: Sedra/Smith).






## Diode circuit example

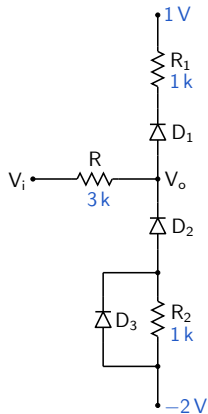


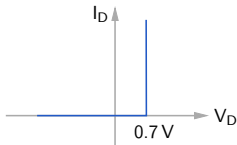Plot  $V_o$  versus  $V_i$  (Ref: Sedra/Smith).




It is easier to find the status (on/off) of each diode w. r. t.  $V_o$ .


## Diode circuit example

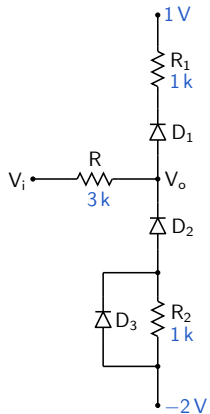

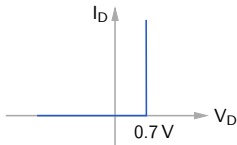
Plot  $V_o$  versus  $V_i$  (Ref: Sedra/Smith).



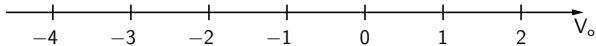
It is easier to find the status (on/off) of each diode w. r. t.  $V_o$ .




## Diode circuit example

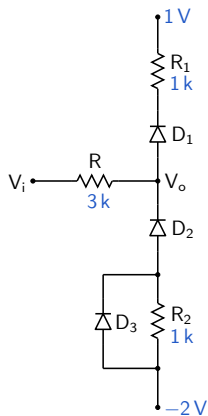

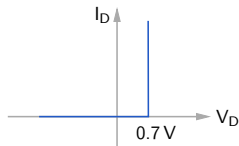
Plot  $V_o$  versus  $V_i$  (Ref: Sedra/Smith).



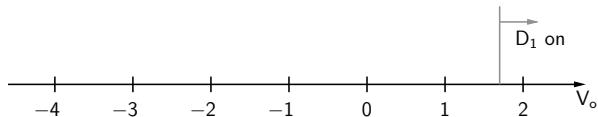
It is easier to find the status (on/off) of each diode w. r. t.  $V_o$ .




## Diode circuit example

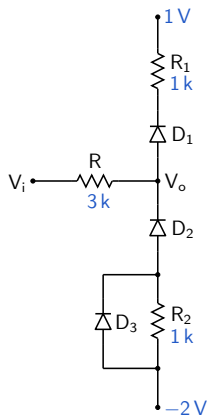

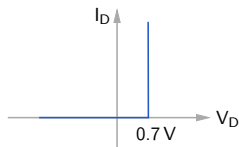
Plot  $V_o$  versus  $V_i$  (Ref: Sedra/Smith).



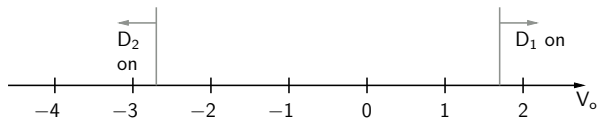
It is easier to find the status (on/off) of each diode w. r. t.  $V_o$ .




## Diode circuit example


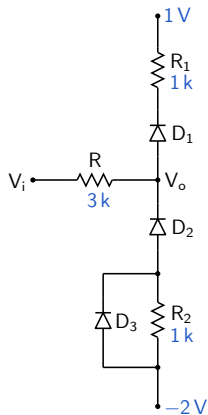



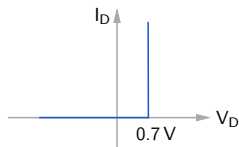
Plot  $V_o$  versus  $V_i$  (Ref: Sedra/Smith).



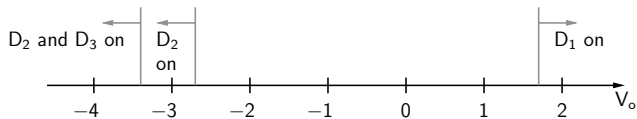It is easier to find the status (on/off) of each diode w. r. t.  $V_o$ .





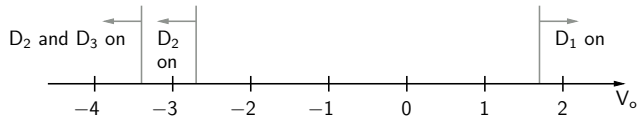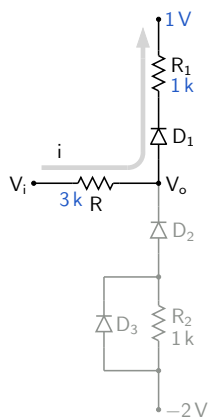

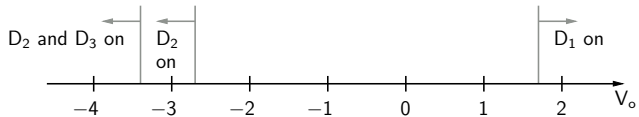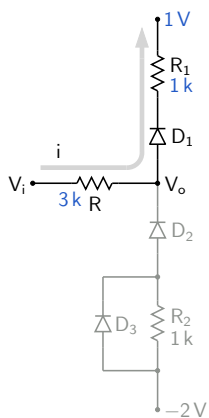

When  $D_1$  just starts conducting,
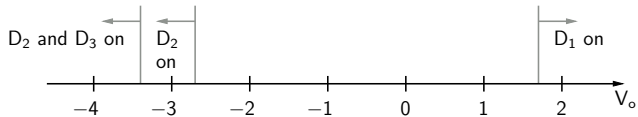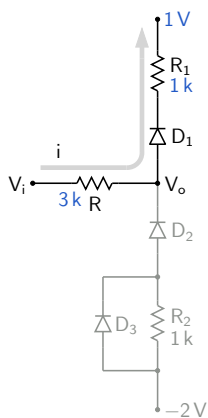
$$V_o = 1.7V, i \approx 0 \rightarrow V_i = 1.7V$$





When  $D_1$  just starts conducting,

$$V_o = 1.7\text{ V}, i \approx 0 \rightarrow V_i = 1.7\text{ V}$$
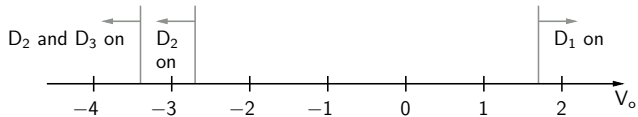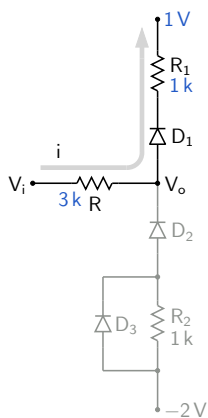
$$\text{For } V_i > 1.7\text{ V, } V_o = 1.7 + \left( \frac{V_i - 1.7}{R + R_1} \right) R_1$$







When  $D_1$  just starts conducting,

$$V_o = 1.7\text{V}, i \approx 0 \rightarrow V_i = 1.7\text{V}$$

$$\text{For } V_i > 1.7\text{V}, V_o = 1.7 + \left( \frac{V_i - 1.7}{R + R_1} \right) R_1$$
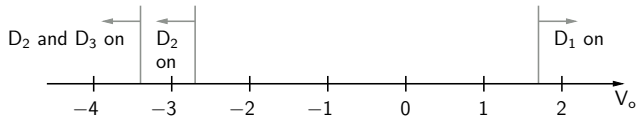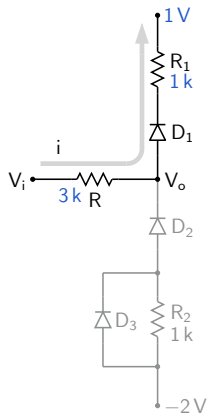
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1}{4}$$





When  $D_1$  just starts conducting,


$$V_o = 1.7\text{V}, i \approx 0 \rightarrow V_i = 1.7\text{V}$$

$$\text{For } V_i > 1.7\text{V}, V_o = 1.7 + \left( \frac{V_i - 1.7}{R + R_1} \right) R_1$$
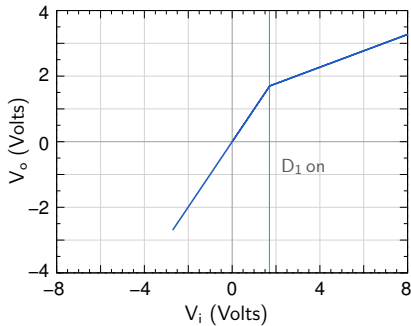
$$\text{Slope } \frac{dV_o}{dV_i} = \frac{R_1}{R + R_1} = \frac{1}{4}$$




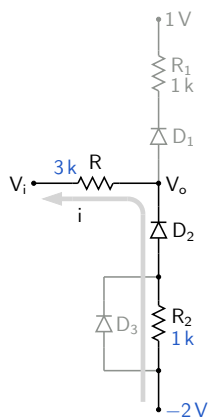

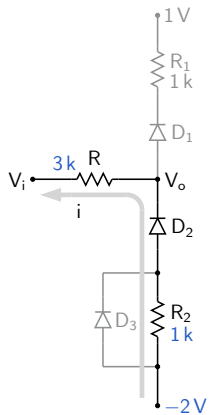

When  $D_2$  just starts conducting,


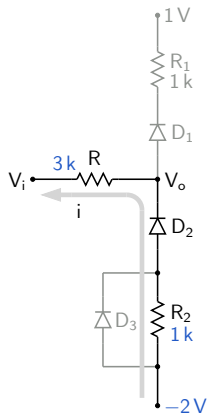
$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$



When  $D_2$  just starts conducting,

$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$
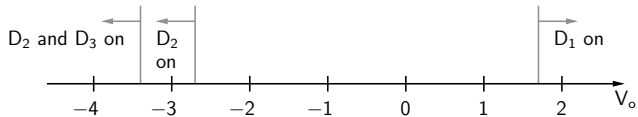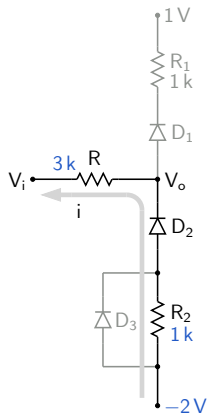
$$\text{For } V_i < -2.7V, V_o = V_i + \left( \frac{-2.7 - V_i}{R + R_2} \right) R$$




When  $D_2$  just starts conducting,

$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$

$$\text{For } V_i < -2.7V, V_o = V_i + \left( \frac{-2.7 - V_i}{R + R_2} \right) R$$
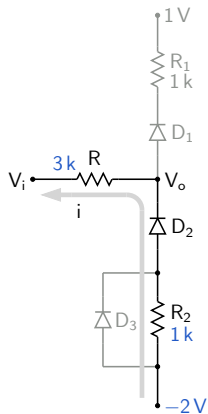
$$\text{Slope } \frac{dV_o}{dV_i} = 1 - \frac{R}{R + R_2} = \frac{R_2}{R + R_2} = \frac{1}{4}$$






When  $D_2$  just starts conducting,

$$V_o = -2.7V, i \approx 0 \rightarrow V_i = -2.7V$$



$$\text{For } V_i < -2.7V, V_o = V_i + \left( \frac{-2.7 - V_i}{R + R_2} \right) R$$
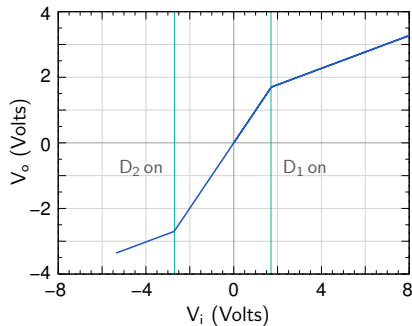
$$\text{Slope } \frac{dV_o}{dV_i} = 1 - \frac{R}{R + R_2} = \frac{R_2}{R + R_2} = \frac{1}{4}$$



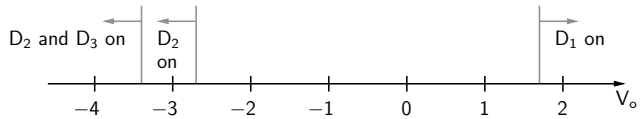
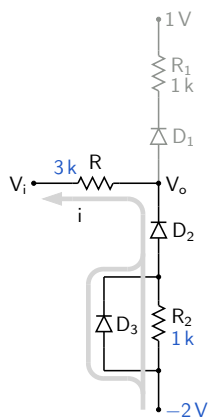




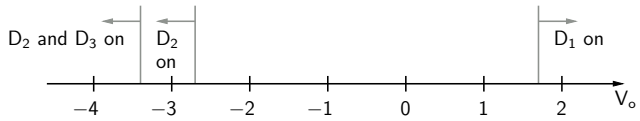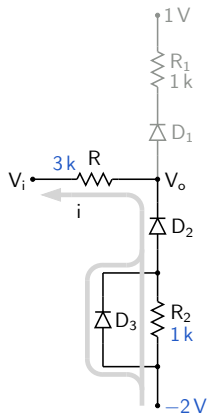

When  $D_3$  just starts conducting,

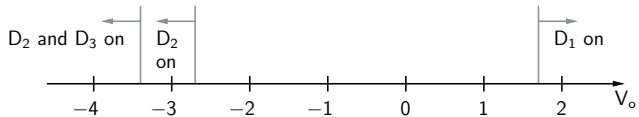
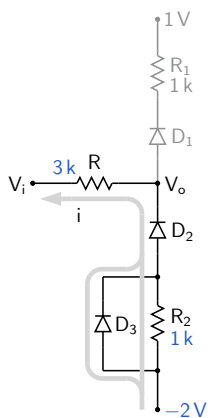
$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7 \text{ V} \rightarrow V_i = -5.5 \text{ V}$$



When  $D_3$  just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7 \text{ V} \rightarrow V_i = -5.5 \text{ V}$$
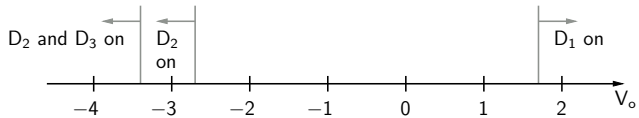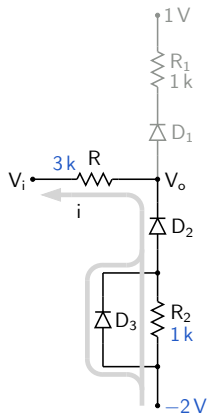
$$V_o = -2 - 0.7 - 0.7 = -3.4 \text{ V}$$





When  $D_3$  just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7 \text{ V} \rightarrow V_i = -5.5 \text{ V}$$

$$V_o = -2 - 0.7 - 0.7 = -3.4 \text{ V}$$

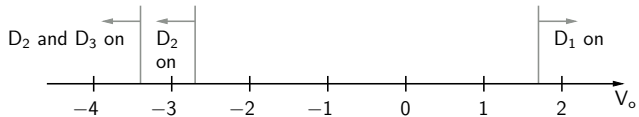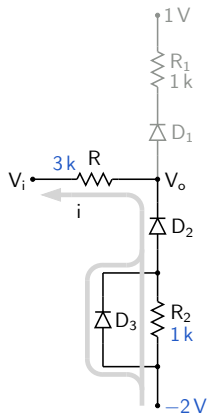For  $V_i < -5.5 \text{ V}$ ,  $V_o = -3.4 \text{ V}$  (constant)






When  $D_3$  just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7 \text{ V} \rightarrow V_i = -5.5 \text{ V}$$

$$V_o = -2 - 0.7 - 0.7 = -3.4 \text{ V}$$

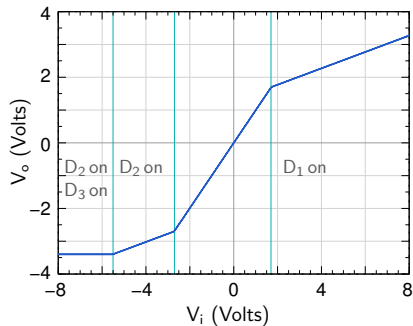For  $V_i < -5.5 \text{ V}$ ,  $V_o = -3.4 \text{ V}$  (constant)



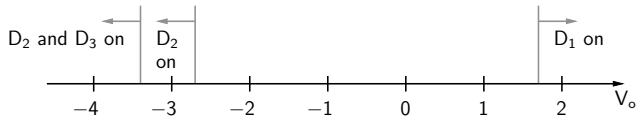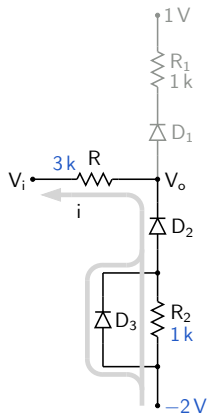


When  $D_3$  just starts conducting,

$$R_2 \frac{(-2.7 - V_i)}{R + R_2} = 0.7 \text{ V} \rightarrow V_i = -5.5 \text{ V}$$

$$V_o = -2 - 0.7 - 0.7 = -3.4 \text{ V}$$

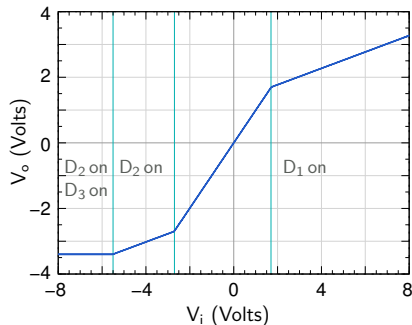
For  $V_i < -5.5 \text{ V}$ ,  $V_o = -3.4 \text{ V}$  (constant)




SEQUEL file:


ee101\_diode\_circuit.12.sqproj

## Reverse breakdown

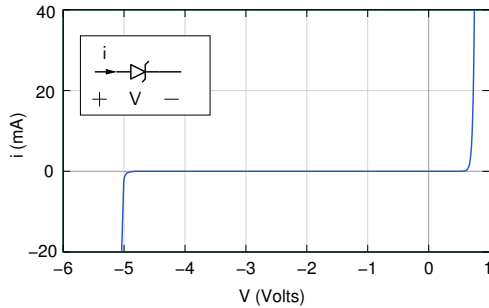

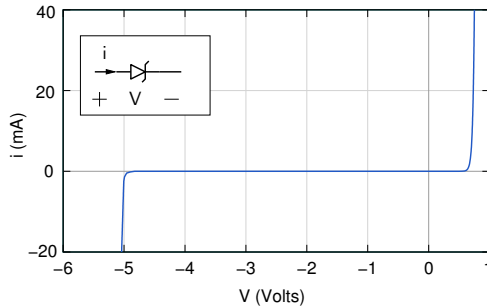


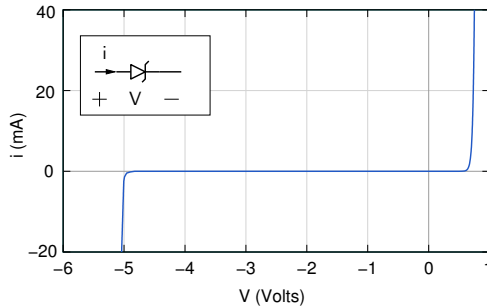- \* In the reverse direction, an ideal diode presents a large resistance for *any* applied voltage.




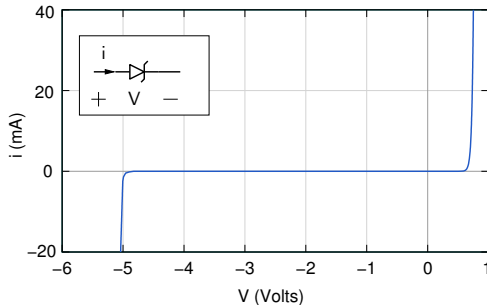
- \* In the reverse direction, an ideal diode presents a large resistance for *any* applied voltage.
- \* A real diode cannot withstand indefinitely large reverse voltages and “breaks down” at a certain voltage called the “breakdown voltage” ( $V_{BR}$ ).







- \* In the reverse direction, an ideal diode presents a large resistance for *any* applied voltage.
- \* A real diode cannot withstand indefinitely large reverse voltages and “breaks down” at a certain voltage called the “breakdown voltage” ( $V_{BR}$ ).
- \* When the reverse bias  $V_R > V_{BR}$  (i.e.,  $V < -V_{BR}$ ), the diode allows a large amount of current. If the current is not constrained by the external circuit, the diode would get damaged.

## Reverse breakdown

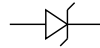
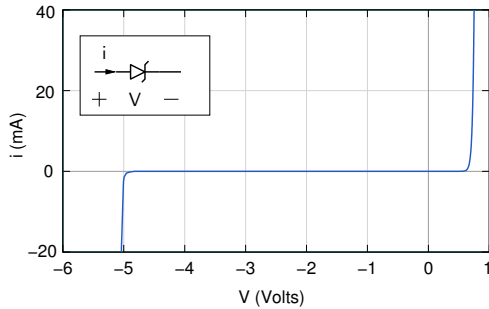


Symbol for a Zener diode

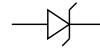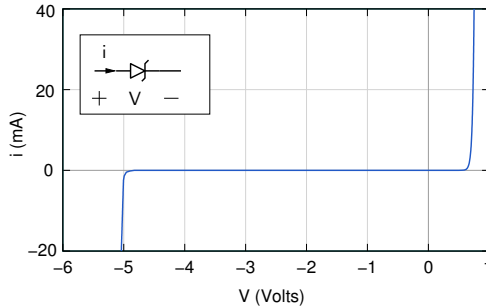



Symbol for a Zener diode

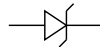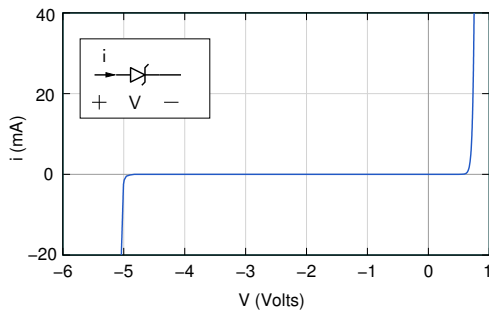- \* A wide variety of diodes is available, with  $V_{BR}$  ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.





Symbol for a Zener diode

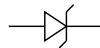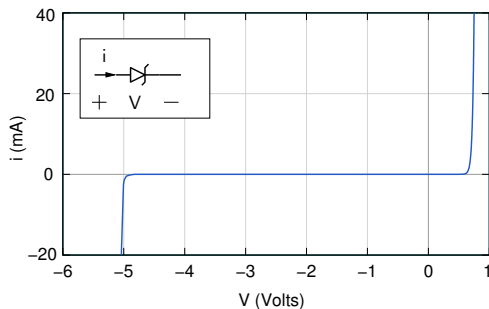- \* A wide variety of diodes is available, with  $V_{BR}$  ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.
- \* Diodes with high  $V_{BR}$  are generally used in power electronics applications and are therefore also designed to carry a large forward current (tens or hundreds of Amps).



Symbol for a Zener diode


- \* A wide variety of diodes is available, with  $V_{BR}$  ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.
- \* Diodes with high  $V_{BR}$  are generally used in power electronics applications and are therefore also designed to carry a large forward current (tens or hundreds of Amps).
- \* Typically, circuits are designed so that the reverse bias across any diode is less than the  $V_{BR}$  rating for that diode.

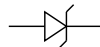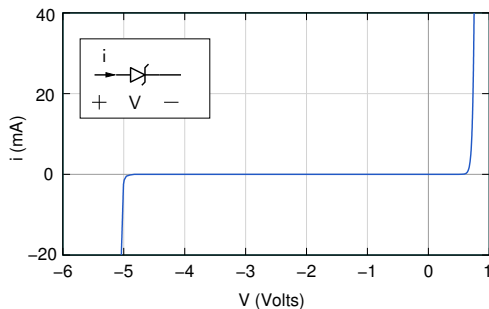


Symbol for a Zener diode

- \* A wide variety of diodes is available, with  $V_{BR}$  ranging from a few Volts to a few thousand Volts! Generally, higher the breakdown voltage, higher is the cost.
- \* Diodes with high  $V_{BR}$  are generally used in power electronics applications and are therefore also designed to carry a large forward current (tens or hundreds of Amps).
- \* Typically, circuits are designed so that the reverse bias across any diode is less than the  $V_{BR}$  rating for that diode.
- \* “Zener” diodes typically have  $V_{BR}$  of a few Volts, which is denoted by  $V_Z$ . They are often used to limit the voltage swing in electronic circuits.
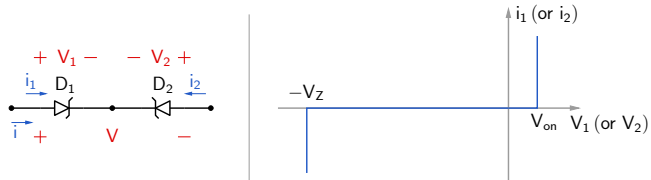
## Two Zener diodes connected "back-to-back"



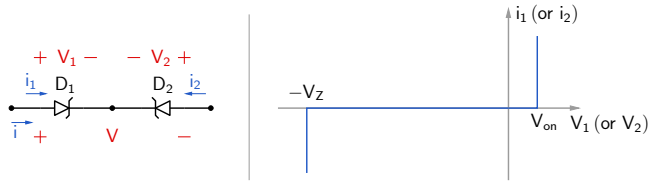
## Two Zener diodes connected “back-to-back”



\*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction



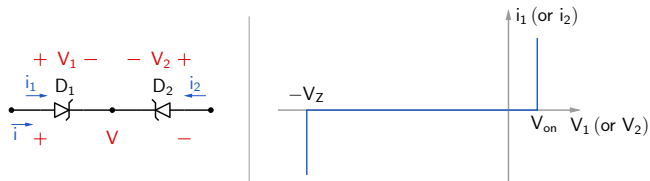
## Two Zener diodes connected “back-to-back”




- \*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction  
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$ .
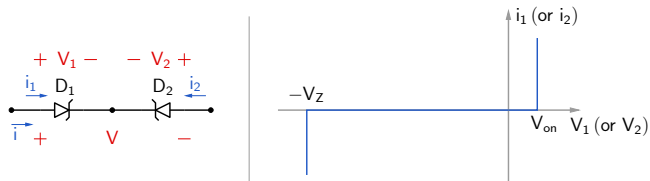
## Two Zener diodes connected “back-to-back”



- \*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction  
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$ .  
Total voltage drop  $V = V_1 - V_2 = V_{on} + V_Z$ .
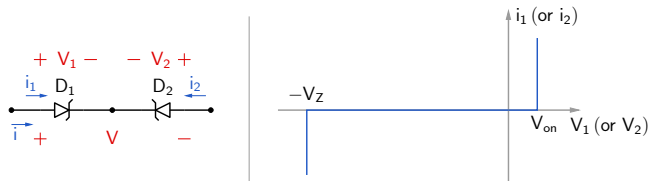
## Two Zener diodes connected “back-to-back”




\*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction

$\rightarrow V_1 = V_{on}, V_2 = -V_Z.$

Total voltage drop  $V = V_1 - V_2 = V_{on} + V_Z.$


Example:  $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}.$
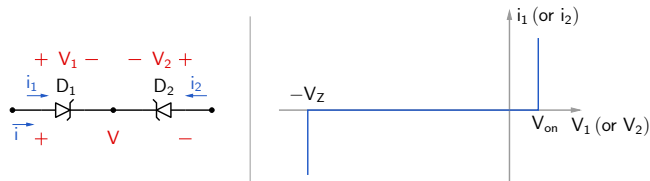
## Two Zener diodes connected “back-to-back”



- \*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction  
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$ .  
Total voltage drop  $V = V_1 - V_2 = V_{on} + V_Z$ .  
Example:  $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$ .
- \*  $i < 0 \rightarrow D_1$  in reverse conduction,  $D_2$  in forward conduction
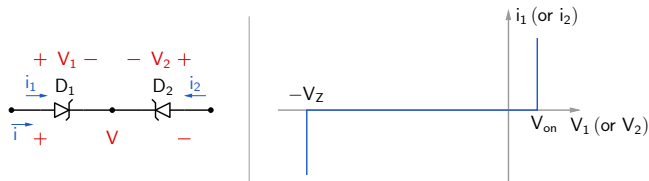
## Two Zener diodes connected “back-to-back”



- \*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction

$$\rightarrow V_1 = V_{on}, V_2 = -V_Z.$$


$$\text{Total voltage drop } V = V_1 - V_2 = V_{on} + V_Z.$$

$$\text{Example: } V_{on} = 0.7 \text{ V}, V_Z = 5 \text{ V} \rightarrow V = 5.7 \text{ V}.$$

- \*  $i < 0 \rightarrow D_1$  in reverse conduction,  $D_2$  in forward conduction

$$\rightarrow V_1 = -V_Z, V_2 = V_{on}.$$
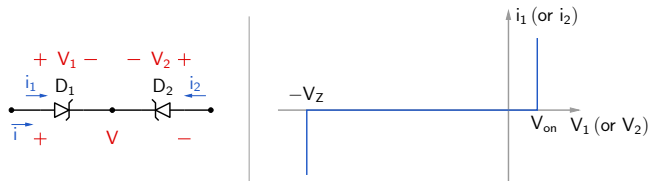
## Two Zener diodes connected “back-to-back”



- \*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction

$$\rightarrow V_1 = V_{on}, V_2 = -V_Z.$$

$$\text{Total voltage drop } V = V_1 - V_2 = V_{on} + V_Z.$$


$$\text{Example: } V_{on} = 0.7 \text{ V}, V_Z = 5 \text{ V} \rightarrow V = 5.7 \text{ V}.$$

- \*  $i < 0 \rightarrow D_1$  in reverse conduction,  $D_2$  in forward conduction

$$\rightarrow V_1 = -V_Z, V_2 = V_{on}.$$


$$\text{Total voltage drop } V = V_1 - V_2 = -V_Z - V_{on} = -(V_Z + V_{on}) = -5.7 \text{ V}.$$
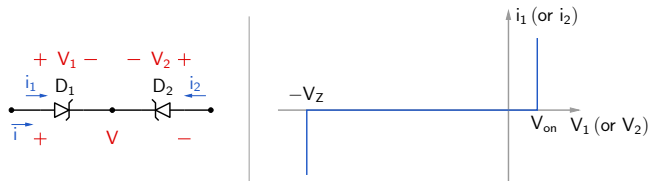
## Two Zener diodes connected “back-to-back”




- \*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction  
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$ .  
Total voltage drop  $V = V_1 - V_2 = V_{on} + V_Z$ .  
Example:  $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$ .
- \*  $i < 0 \rightarrow D_1$  in reverse conduction,  $D_2$  in forward conduction  
 $\rightarrow V_1 = -V_Z, V_2 = V_{on}$ .  
Total voltage drop  $V = V_1 - V_2 = -V_Z - V_{on} = -(V_Z + V_{on}) = -5.7\text{ V}$ .
- \* For  $-(V_Z + V_{on}) < V < (V_Z + V_{on})$ , conduction is not possible  $\rightarrow i = 0$ .
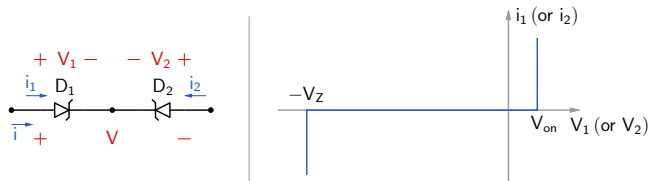
## Two Zener diodes connected “back-to-back”




- \*  $i > 0 \rightarrow D_1$  in forward conduction,  $D_2$  in reverse conduction  
 $\rightarrow V_1 = V_{on}, V_2 = -V_Z$ .  
 Total voltage drop  $V = V_1 - V_2 = V_{on} + V_Z$ .  
 Example:  $V_{on} = 0.7\text{ V}, V_Z = 5\text{ V} \rightarrow V = 5.7\text{ V}$ .
- \*  $i < 0 \rightarrow D_1$  in reverse conduction,  $D_2$  in forward conduction  
 $\rightarrow V_1 = -V_Z, V_2 = V_{on}$ .  
 Total voltage drop  $V = V_1 - V_2 = -V_Z - V_{on} = -(V_Z + V_{on}) = -5.7\text{ V}$ .
- \* For  $-(V_Z + V_{on}) < V < (V_Z + V_{on})$ , conduction is not possible  $\rightarrow i = 0$ .

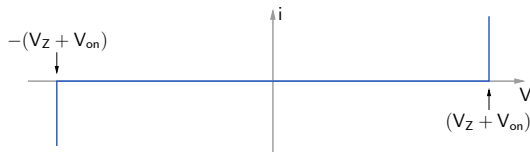



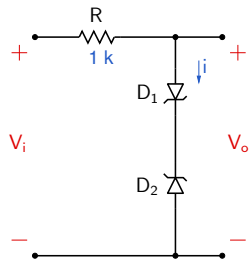
## Diode circuit example (voltage limiter)



$$V_{\text{on}} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot  $V_o$  versus  $V_i$ .

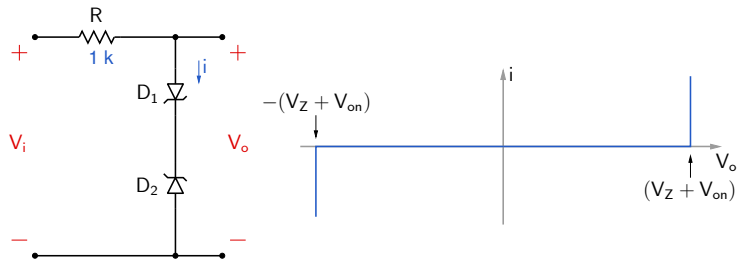
## Diode circuit example (voltage limiter)



$$V_{on} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot  $V_o$  versus  $V_i$ .
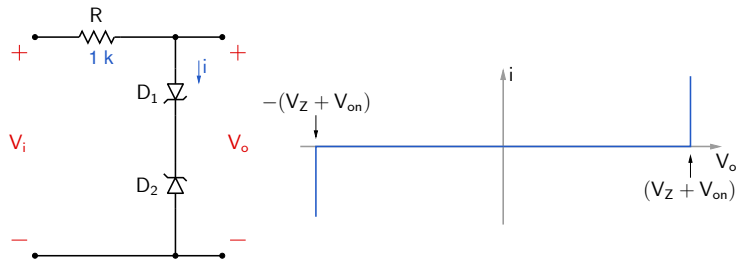
## Diode circuit example (voltage limiter)




$$V_{on} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot  $V_o$  versus  $V_i$ .



\* For  $-5.7\text{ V} < V_i < 5.7\text{ V}$ , no conduction is possible  $\rightarrow V_o = V_i$ .
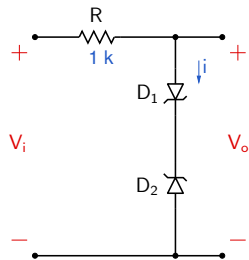
## Diode circuit example (voltage limiter)




$$V_{\text{on}} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot  $V_o$  versus  $V_i$ .

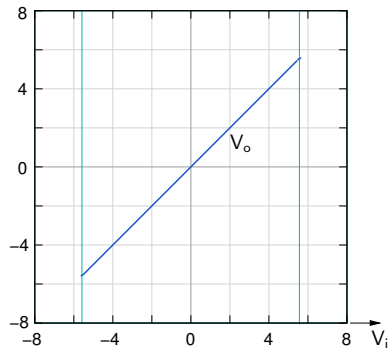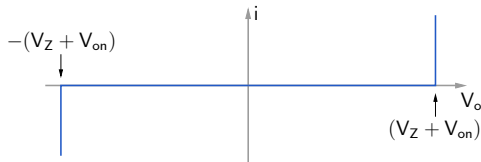



\* For  $-5.7\text{ V} < V_i < 5.7\text{ V}$ , no conduction is possible  $\rightarrow V_o = V_i$ .
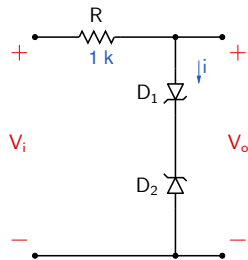
## Diode circuit example (voltage limiter)




$$V_{\text{on}} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot  $V_o$  versus  $V_i$ .

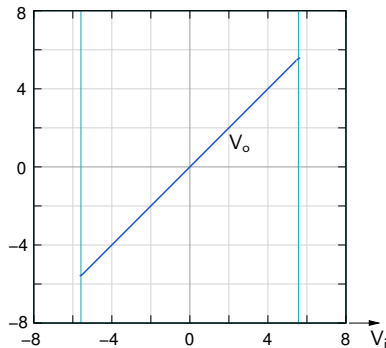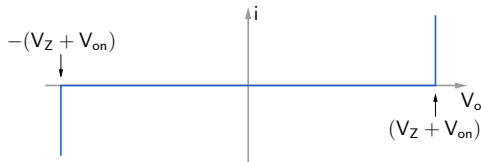



- \* For  $-5.7\text{ V} < V_i < 5.7\text{ V}$ , no conduction is possible  $\rightarrow V_o = V_i$ .
- \* For  $V_i > 5.7\text{ V}$ ,  $D_1$  is forward-biased,  $D_2$  is reverse-biased, and  $V_o = (V_{\text{on}} + V_Z)$ . The excess voltage  $(V_i - (V_{\text{on}} + V_Z))$  drops across  $R$ .
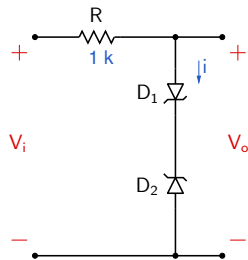
## Diode circuit example (voltage limiter)




$$V_{\text{on}} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot  $V_o$  versus  $V_i$ .

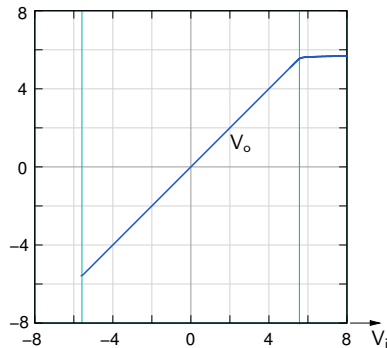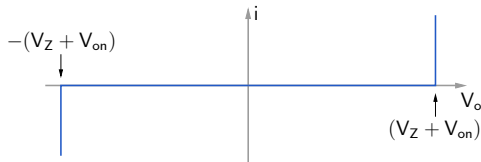



- \* For  $-5.7\text{ V} < V_i < 5.7\text{ V}$ , no conduction is possible  $\rightarrow V_o = V_i$ .
- \* For  $V_i > 5.7\text{ V}$ ,  $D_1$  is forward-biased,  $D_2$  is reverse-biased, and  $V_o = (V_{\text{on}} + V_Z)$ . The excess voltage  $(V_i - (V_{\text{on}} + V_Z))$  drops across  $R$ .
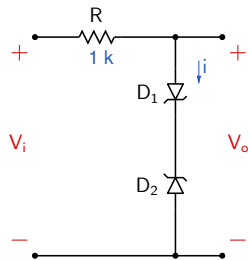
## Diode circuit example (voltage limiter)




$$V_{\text{on}} = 0.7\text{ V}, V_Z = 5\text{ V}.$$

Plot  $V_o$  versus  $V_i$ .

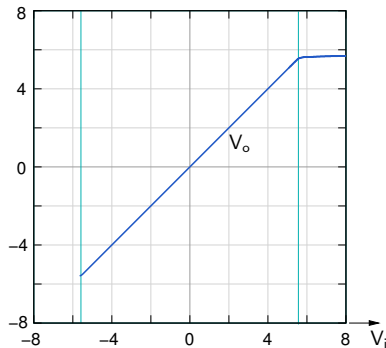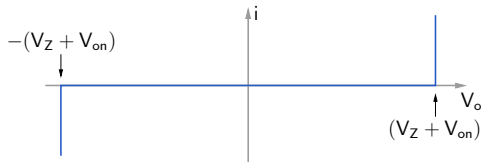



- \* For  $-5.7\text{ V} < V_i < 5.7\text{ V}$ , no conduction is possible  $\rightarrow V_o = V_i$ .
- \* For  $V_i > 5.7\text{ V}$ ,  $D_1$  is forward-biased,  $D_2$  is reverse-biased, and  $V_o = (V_{\text{on}} + V_Z)$ . The excess voltage  $(V_i - (V_{\text{on}} + V_Z))$  drops across  $R$ .
- \* For  $V_i < -5.7\text{ V}$ ,  $D_2$  is forward-biased,  $D_1$  is reverse-biased, and  $V_o = -(V_{\text{on}} + V_Z)$ . The excess voltage  $(-V_i - (V_{\text{on}} + V_Z))$  drops across  $R$ .
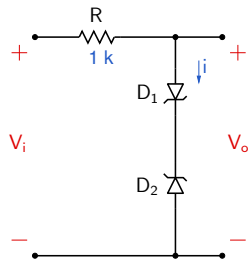
## Diode circuit example (voltage limiter)



$$V_{on} = 0.7 \text{ V}, V_Z = 5 \text{ V}.$$

Plot  $V_o$  versus  $V_i$ .

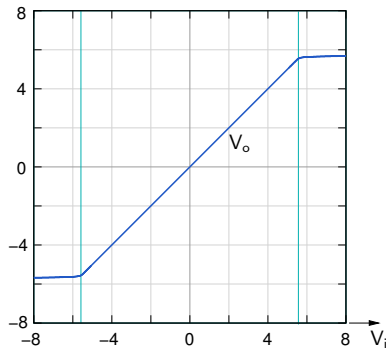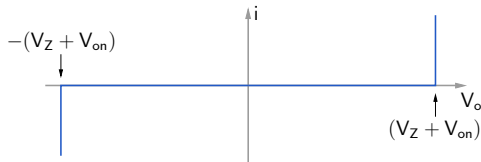

- \* For  $-5.7 \text{ V} < V_i < 5.7 \text{ V}$ , no conduction is possible  $\rightarrow V_o = V_i$ .
- \* For  $V_i > 5.7 \text{ V}$ ,  $D_1$  is forward-biased,  $D_2$  is reverse-biased, and  $V_o = (V_{on} + V_Z)$ . The excess voltage  $(V_i - (V_{on} + V_Z))$  drops across  $R$ .
- \* For  $V_i < -5.7 \text{ V}$ ,  $D_2$  is forward-biased,  $D_1$  is reverse-biased, and  $V_o = -(V_{on} + V_Z)$ . The excess voltage  $(-V_i - (V_{on} + V_Z))$  drops across  $R$ .